

Notes on BIOMEDE 211, or:
Circuits, Systems, & Signals
in Biomedical Engineering

Barry Belmont

February 28, 2019

Contents

0.1	How can I print off and use this document?	iv
0.2	How can I contribute to GitHub?	v
0.3	Who comprises this class and how can they be reached? . . .	vi
0.3.1	The Captain at the helm	vi
0.3.2	The A-Team	vi
0.3.3	You, yourselves	vi
0.4	What is this class about?	viii
0.5	When and where does this class meet?	ix
0.6	What is required for this class?	ix
0.6.1	Writing materials	ix
0.6.2	Access to the internet periodically	ix
0.6.3	A textbook of some kind	ix
0.7	What determines the grade?	ix
0.7.1	The abject material of the the thing	ix
0.7.2	The largely arbitrary, but nevertheless significant scale by which the grade will be measured by the instructors	x
0.7.3	The policy regarding missed chances, do overs, and dishonesty	x
0.8	What are the objectives of this class?	xi
0.9	What are the outcomes I can expect of myself from this class?	xi

I	Circuits	1
1	I. Potential, current, energy, conservation	3
1.1	What is electricity?	3
1.2	Charge	3
1.3	Current	4
1.3.1	The directionality of current	4
1.3.2	The at times deadly serious nature of current	5

1.3.3	The “speed” of current	5
1.4	Potential (difference)	6
1.5	Power	7
1.6	Energy	7
1.7	Conservation	8
1.8	Worksheet	9
1.8.1	Problem 1, constant charge through a cross-section . .	9
1.8.2	Problem 2, arbitrary charge through a cross-section .	9
1.8.3	Problem 3, a ”tera”ble puzzle	9
1.8.4	Problem 4, power necessary to run a pacemaker	9
1.8.5	Problem 5, energy needed to excite a neuron	9
1.8.6	Problem 6, a thump to the chest	10
2	An introduction: II. Circuit elements	11
2.1	Active v. passive	11
2.2	Ohm’s Law and what it means	11
2.3	Sources	12
2.4	Resistors	12
2.4.1	Resistance, R	12
2.4.2	Resistivity, ρ	13
2.4.3	Conductance	13
2.5	Capacitors	14
2.5.1	Its time varying behavior	14
2.5.2	Charge accumulation	15
2.5.3	A simple example	15
2.6	Inductors	15
2.7	Impedance	16
2.7.1	A quick note on “imaginary” numbers	17
2.8	Equivalent impedance	17
2.8.1	Impedances in general	18
2.8.2	Resistors	18
2.8.3	Capacitors	18
2.8.4	Delta-Wye (Δ - Y) transformations	19
2.8.5	A few examples	19
2.9	Grounds	20
2.10	Conductors	20
2.11	Operational amplifiers (“Op-amps”)	20
2.12	Diodes	20
2.13	Switches	20
2.14	Transistors	21

2.15	Transformers	21
2.16	Worksheet	22
2.16.1	Problem 1, expressing power in ohms	22
2.16.2	Problem 2, a couple toaster based problems	22
2.16.3	Problem 3, currently conducting power	22
2.16.4	Problem 4, conductance of a sodium channel	22
2.16.5	Problem 5, resistance of a simple tissue	22
3	An introduction: III. Operational amplifiers	23
3.1	Some details	24
3.2	Some rules	25
3.3	Some conveniences	25
3.4	Some examples	26
3.4.1	Inverting amplifier	26
3.4.2	Non-inverting amplifier	27
3.4.3	Voltage follower	28
3.4.4	Summing amplifier	28
3.4.5	Differential amplifier (as homework)	28
4	Circuit analysis: I. Nodal analysis	29
4.1	Nodes and branches	30
4.1.1	The Seven Bridges of Königsberg	30
4.1.2	Independence	31
4.1.3	Fundamental theorem of network topology	31
4.2	Kirchhoff's Laws	32
4.2.1	Kirchhoff's Current Law	32
4.2.2	Kirchhoff's Voltage Law	33
4.2.3	A few examples	33
4.3	Nodal analysis	36
4.3.1	The procedure	36
4.4	Solving simultaneous equations	37
4.4.1	Cramer's Rule	37
4.5	Worksheet	40
4.5.1	Problem 1, KCL at a few nodes	40
4.5.2	Problem 2, matrix notation	40
4.5.3	Problem 3, Cramer's rule	40
4.5.4	Problem 4, Straight to the matrix	40

5	Circuit analysis: II. Mesh analysis	41
5.1	Clarifications on the homework	42
5.2	Mesh analysis	42
5.3	Steps of mesh analysis	42
5.3.1	Important condition for use	42
5.4	An example	43
5.5	Another example	44
5.5.1	Solving it one way	44
5.5.2	Solving it another	45
5.6	Yet another example	46
5.7	Writing mesh equations directly in matrix form	47
6	Circuit analysis: III. Supernodes and supermeshes	49
6.1	A review of nodal and mesh analysis	50
6.1.1	Nodal analysis	50
6.2	Nodal analysis with an independent current source	51
6.3	A brief review of Cramer's rule	53
6.4	Nodal analysis with voltage sources, Supernodes	54
6.5	Nodal analysis with controlled sources	56
6.6	Mesh analysis with current sources	57
6.7	Mesh analysis with controlled sources, Supermeshes	57
7	Circuit analysis: IV. Circuit theorems	59
7.1	Circuit theorems	60
7.2	Linearity	60
7.3	Superposition	61
7.4	Source transformation	63
7.5	Thevenin equivalents	63
7.5.1	An example	65
7.6	Norton equivalents	66
7.6.1	An example	66
7.7	Equivalents with dependents	68
7.8	A step-by-step procedure	69
8	A review of the material so far	71
8.1	A set of exercises in preparation of the first Glorified Quiz . . .	71
8.2	Problem 1 on basic impedance	80
8.3	Problem 2 on basic knowledge	80
8.4	Problem 3 on current and potential	80
8.5	Problem 4 on transresistance amplification or bioamplification	81

8.6	Problem 5 on equivalent impedance	81
8.7	Problem 6 on differential amplification	81
8.8	Problem 7 on counting cells	81
8.9	Problem 8 on your own	82
8.10	Problem 9 also on your own	82
8.11	Problem 10 on miscellanea	82
8.12	Useful equations in alphabetical order	83

II Systems 85

9 The Laplace Transform: I. What it is and why it is important 87

9.1	Euler's formula, Euler's identity	88
9.2	The Laplace transform	89
9.3	The Laplace transform of 1	90
9.4	The s -plane	91
9.5	The linearity of the Laplace transform	93
9.6	The Laplace transform of e^{at}	93
9.7	The Laplace transform of dx/dt	94
9.8	The Laplace transform of \sin	96
9.9	The Laplace transform of $\int_0^t x(u)du$	96
9.10	The Laplace transform in RLC circuits	97
9.10.1	Resistors	97
9.10.2	Inductors	97
9.10.3	Capacitors	98
9.10.4	RLC circuits	99

10 The Laplace Transform: II. How to use it 101

10.1	A brief review	102
10.2	Two important places, zeros and poles	103
10.3	The general form of just about all systems	104
10.3.1	Undamped systems	104
10.3.2	Underdamped systems	105
10.3.3	Critically damped systems	105
10.3.4	Overdamped systems	105
10.4	"Inverting" the Laplace transform	106
10.4.1	A convenient way of doing it	106
10.5	Worksheet	107
10.5.1	Problem 1	107

10.5.2 Problem 2	107
10.5.3 Problem 3	107
10.5.4 Problem 4	108
10.5.5 Problem 5	108
11 Circuits as ODEs: I. First-order	109
11.1 Source-free RC circuits	109
11.1.1 One resistor, one capacitor	109
11.1.2 Two or more resistors and/or capacitors	109
11.2 Source-free “active” circuits	109
11.3 First-order systems with sources	109
11.4 Several singular functions	109
11.4.1 Unit step function, $u(t - t_0) = 1, t > t_0$	109
11.4.2 Unit impulse function, $\delta(t) = du(t)/dt$	109
11.4.3 Unit ramp function, $r(t) = \int u(t)dt$	109
12 Circuits as ODEs: II. Second-order	111
12.1 A series RLC circuit	111
13 System response: I. Convolution	113
13.1 An introduction to thinking in systems	114
13.2 Pulse and impulse	114
13.3 Convolution	115
13.3.1 Convolution as a series of weighted sums	118
13.3.2 A few properties of convolution	118
13.3.3 The Laplace transform of a convolution	118
13.4 A few examples	119
13.4.1 Convolution of an exponential and a sin function . . .	119
14 System response: II. Stability	121
14.1 An introduction	121
14.1.1 What do we mean by stability?	121
14.2 Undamped, $\zeta = 0$	121
14.3 Underdamped, $0 < \zeta < 1$	121
14.4 Overdamped, $\zeta > 1$	121
III & Signals	123
15 System response: III. The frequency domain	125

16 System response: IV. Filters	127
17 System response: V. Feedback; Homework IV	129
IV in Biomedical Engineering	133
18 Bioelectricity: I. Passive properties	135
18.1 Modeling biological material with a simple circuit, $R_1 + (R_2 C)$	135
18.2 Resistance-Reactance Plane	135
18.3 What can we do with this information?	135
19 Bioelectricity: II. Active properties	137
20 Bioelectricity: III. Measurement	139
21 Digital circuits: I. Discretization	141
22 Digital circuits: II. Logic; Homework V	143
23 Happenstance: A few BME specific situations	145
24 Circumstance: A few BME specific standards	147
25 A philosophy of circuits, systems, and signals; Homework VI	149
V Assignments	153
1.1 Problem 1	155
1.2 Problem 2	156
1.3 Problem 3	156
1.4 Problem 4	156
1.5 Problem 5	156
1.6 Problem 6	156
1.7 Problem 7	157
1.8 Problem 8	157
1.9 Problem 9	157
1.10 Problem 10	158
2.1 Problem 1	159
2.2 Problem 2	160
2.3 Problem 3	160

2.4	Problem 4	161
2.5	Problem 5	161
2.6	Problem 6	161
2.7	Problem 7	162
2.8	Problem 8	162
2.9	Problem 9	163
2.10	Problem 10	163
3.1	Problem 1 on mathematical proficiency	165
3.2	Problem 2 on poles and zeros, exponentially	166
3.3	Problem 3 on the stability of geopolitical systems	166
3.4	Problem 4 on a circuit as a differential equation	167
3.5	Problem 5 on poles and zeros, applicably	168

0.1 How can I print off and use this document?

Frankly, in just about any way thats useful to you. I am going to try something here, where I will try to make more or less the entirety of the notes associated with the Winter 2019 semester of BIOMEDE 211, Circuits, Systems, and Signals in Biomedical Engineering, to you, dear reader.

Please dont plagiarize this. If you were raised right, you ought to know what that is. If youd like my judgment on any sort of action, my opinions can be laid bare.

The first assignment I am giving you (worth 4% of your grade and which must be completed by the end of the semester) is to figure out where this document is located online, download it, print it off, sign your name to it, and get it to me. If you know who I am, I would expect a competent engineer to find that without much to-do about it. Start with Google, go from there. Further, for those in the class, BIOMEDE 211, Winter 2019, you must join Github and make at least four substantive contributions to this repository. The term all you engineers (and lawyers) cant wait to parse is substantive to which I will always enter a judgment which I deem final in this class, and I am ever in favor of beneficence over stricture. So, just help out the class in a way you think is helpful and watch those around you do the same. Failure to contribute to this living document by the end of the semester for those in this class will result in a loss of up to 4% of one's total grade outright.

0.2 How can I contribute to GitHub?

Follow these general steps to propose a change to this online document:

1. Create a GitHub account

This should be rather self-explanatory. Use your e-mail account and verify it to be able to edit. You should proceed with the following steps while logged onto your account.

2. Find Dr. Belmont's GitHub page and go to the biomed-211-w19 repository ("repo"). Then click on the biomed-211-w19.tex file.

3. Edit the file

You will find a small pencil icon on the right side of the page. Click on this to create your own branch ("forking"), and edit the file as you wish.

4. Propose file change

After making your changes, you should scroll to the bottom of the page, find the message box that says, 'Propose file change', and fill it out. The first line should say what you have updated and can be explained in the description.

5. Create pull request

After finishing your file, you will be brought to a page that displays what you have modified on the original document. Press the green 'Create pull request' button to let Dr. Belmont know that you want to create a change. Once he has approved via his own GitHub account, your changes should now be in the updated master branch!

0.3 Who comprises this class and how can they be reached?

0.3.1 The Captain at the helm

Barry Belmont
Wednesdays 11:00 a.m. — 1:00 p.m., 2130 LBME
belmont@umich.edu

0.3.2 The A-Team

Annabelle St. Pierre
Wednesdays 5:00 p.m. — 6:30 p.m., UGLI basement
astpierr@umich.edu

Alice Tracey
Wednesdays 4:00 p.m. — 5:00 p.m., UGLI basement
atracey@umich.edu

0.3.3 You, yourselves

In this class, we will be learning a lot from each other. You are encouraged to learn from one another. You are encouraged to talk to one another. You are encouraged to share ideas and at times data. You are not encouraged and are hereby expressly forbidden to submit the work of another as your own. If you get help from others, you will put their name on it somewhere. Too much of this and you are committing plagiarism, not enough and you are committing fraud. Please be honest and let's all learn together.

1. Kristian A.
2. Matt A.
3. Rayna B.
4. Ellianna B.
5. Megan B.
6. Ashley B.

7. Dawn C.
8. Weihong C.
9. Caila C.
10. Jenna D.
11. Sandra D.
12. James G.
13. Natalie H.
14. Yazmin H.
15. Felicia H.
16. Isabel H.
17. Danica J.
18. Surabhi J.
19. David K.
20. Erica K.
21. Eunjeong L.
22. Annie L.
23. Ian M.
24. Madelynn M.
25. Devak N.
26. Likitha N.
27. Bree P.
28. Neelay P.
29. Matei P.
30. Shaunak P.

- 31. Francesca Q.
- 32. Raahul R.
- 33. Abigail R.
- 34. Alexander R.
- 35. Andrew R.
- 36. Elizabeth R.
- 37. Kiana S.
- 38. Ryan S.
- 39. Sydney S.
- 40. Hao S.
- 41. Andrew S.
- 42. Elijah S.
- 43. Cara S.
- 44. Aparna S.
- 45. Alec S.
- 46. Madison W.
- 47. Jordyn W.

0.4 What is this class about?

From the course catalog, “Students learn circuits and linear systems concepts necessary for analysis and design of biomedical systems. Theory is motivated by examples from biomedical engineering. Topics covered include electrical circuit fundamentals, operational amplifiers, frequency response, electrical transients, impulse response, transfer functions and convolution, all motivated by circuit and biomedical examples. Elements of continuous time-domain and frequency-domain analytical techniques are developed.”

From your instructor’s heart, ”Youre going to learn the fundamental basis of electricity and its specific applicability to biomedical engineering,

broadly. With this knowledge, you will have a command over a vaster swath of this world than most as you'll know something important about how it works: namely, how human beings push electrons around the world to do some quite interesting things and how those electrons push back. This has relevance to a great many disparate situations: from the swelling of potential as your heart dances in your chest to nearly every source of light you've ever seen sans the sun (and even then...). All this to say, what we do here matters. And we'll aim to do it well."

0.5 When and where does this class meet?

Tuesdays and Thursdays, 12:30 – 2:30 p.m., 1006 DOW

0.6 What is required for this class?

0.6.1 Writing materials

A good pen and some sheets of paper ought to do.

0.6.2 Access to the internet periodically

A good bulk of our class's administration will be done through Canvas. Check it regularly.

0.6.3 A textbook of some kind

Getting more than one perspective on a topic helps most people learn better. As such, in addition to the textbook which you are currently reading, I recommend consulting another electric circuits text. We have, in the past, used *Fundamentals of Electric Circuits*, 6th edition, by Charles Alexander and Matthew Sadiku, which is also used by our EECS brothers and sisters. Digital or hardcopy is fine. As are older editions or equivalents.

0.7 What determines the grade?

0.7.1 The subject material of the thing

Grades are determined essentially through three distinct types of assessment.

- The first and foremost of these are out-of-class based assignments (henceforth, “homework”), individually worth 8 percent, and collectively worth 48 percent of the overall grade.
- The second and secondmost of these are three in-class based assignments (henceforth, “glorious quizzes/exams”), which are worth 12, 12, and 20 percent of the overall grade, respectively.
- The final type is the evaluation of a certain in-class/out-of-class *je-nais se quoi* quality of the participatory student. “Participation” is something I take seriously in my classes and in this class will consist of (1) at least one in-class demonstration of your solutions to problems posed during the lecture period and (2) contribution to this specific document through the GitHub. Each of these forms of participation are worth 4 percent of the grade.

0.7.2 The largely arbitrary, but nevertheless significant scale by which the grade will be measured by the instructors

As this is my second time teaching this course, some calibration (on a per assignment and/or class- wide basis) may be required. That said, I plan on grading this class just as you might expect any other engineering class to do so against the following scale:

$$\begin{aligned} A+ &\geq 97; A \geq 94; A- \geq 90; \\ B+ &\geq 87; B \geq 84; B- \geq 80; \\ C+ &\geq 77; C \geq 74; C- \geq 70; \\ D &\geq 60; F \geq 50 \end{aligned}$$

0.7.3 The policy regarding missed chances, do overs, and dishonesty

- **If you will be absent** for some key assessment (a homework, an exam, participation), let the instructor know ahead of time and we can work something out.
- **If you feel the assessment of your work was wrong, misguided, or unfair**, let the instructor know immediately and specifically (within 48 hours of the assessment being returned) and we will work something out.

- **If you insist at any point on swindling yourself out of an honest education**, please reconsider your decisions to do so (perhaps by discussing the matter with your instructor), otherwise this whole engineering thing for you is not going to work out. You are encouraged to read the Honor Code of the institution to which you are responsible.

0.8 What are the objectives of this class?

1. To generate physical understanding of fundamental circuit and systems concepts.
2. To relate classroom material to real-world applications including selected biomedical systems.
3. To teach students basic circuit and linear systems including transient, frequency response, impulse response, and transfer functions.
4. To introduce mathematical concepts necessary to accomplish the above including convolution, Laplace transforms, and Fourier transforms.

0.9 What are the outcomes I can expect of myself from this class?

1. Learn basic circuit and systems techniques necessary for understanding biomedical instrumentation systems, bioelectrical systems, and medical imaging systems.
2. Develop an insight into systems analysis techniques motivated by development of electrical circuits concepts.
3. Develop an insight into operational amplifier analysis and design techniques as motivated by a series of practical biomedical amplifier designs.
4. Understand mathematical tools necessary for linear systems and circuit analysis/design.

Part I

Circuits

Chapter 1

I. Potential, current, energy, conservation

01/10/2019

Contents

1.1	What is electricity?	3
1.2	Charge	3
1.3	Current	4
1.3.1	The directionality of current	4
1.3.2	The at times deadly serious nature of current	5
1.3.3	The “speed” of current	5
1.4	Potential (difference)	6
1.5	Power	7
1.6	Energy	7
1.7	Conservation	8
1.8	Worksheet	9
1.8.1	Problem 1, constant charge through a cross-section	9
1.8.2	Problem 2, arbitrary charge through a cross-section	9
1.8.3	Problem 3, a ”tera”ble puzzle	9
1.8.4	Problem 4, power necessary to run a pacemaker	9
1.8.5	Problem 5, energy needed to excite a neuron	9
1.8.6	Problem 6, a thump to the chest	10

1.1 What is electricity?

1. A form of energy resulting from the existence of charged particles
2. The physical phenomena arising from the existence, presence, and motion of charged particles
3. Rather ill-defined in common vernacular we will generally avoid its use

1.2 Charge

1. Charge is the property of matter that causes it to experience a force when placed in an electromagnetic field; measured in coulombs (C)
2. Charges are found in nature in discrete, integral multiples of electronic charge: $e = -1.602 \times 10^{-19}$ C (the charge of one electron)
3. **How many electrons are needed to form one coulomb?** (What is the weight of all those electrons?)
4. One byte is eight bits. Bits are essentially a single electron stored in a transistor. **If we were to take all the electrons from one terabyte of well distributed information (equal number of ones and zeros), how many coulombs would we have?**

1.3 Current

1. The time rate of change of charge charges (charged particles) in motion; measured in amperes; defined mathematically as

$$i := dq/dt \tag{1.1}$$

where i is current, q is charge, and t is time

2. Conversely, the total charge transferred over time can be expressed as

$$Q := \int_{t_0}^t i dt \tag{1.2}$$

3. 1 ampere is equal to 1 coulomb/second
4. Direct current, “DC”, is current that remains constant with time
5. Alternating current, “AC”, is current that varies sinusoidally with time

1.3.1 The directionality of current

Ultimately, the direction in which we say "current" flows is largely arbitrary. As arbitrary as choosing one type of charge and calling it "positive" and another "negative". The reason it doesn't matter is that the only consequence of having chosen a "wrong direction" for the current in a given analysis is that we have to switch the sign of the value. Thus, 3 amps in one direction is *the exact same thing* as -3 in the opposite direction.

1. Thanks to Benjamin Franklin we say that current is
 - i. **Positive in the direction in which positively charged particles flow** and
 - ii. **Negative in the direction in which negatively charged particles**
 - iii. We also now know that current results primarily from the movement of negatively charged particles (electrons) and therefore our convention is wrong in one sense, though convenient and entrenched enough that were not liable to change it in our life time (besides, the math comes out the same, and the actual flow of electrons will only matter to us in a few special circumstances, diodes)

1.3.2 The at times deadly serious nature of current

Much of the point of learning this material here is its eventual application by our hands or by the hands of those we work with. Before we put any of this stuff in our hands, we should probably know what is and is not safe.

1. 1 mA, you will feel
2. 10 mA, you will really feel
3. 100 mA, you will likely die
4. 1000 mA, you will definitely die

1.3.3 The "speed" of current

A possible misconception is that the electrons inside a wire travels at the speed of light. The speed of current is actually relatively slow. If one were to imagine an electron starting at the wire next to a light switch in an average classroom, it would take a very long period of time for it to travel to the light itself. The light's immediate reaction to a switch is due to a "hose

effect”; the electrons inside the wire push other electrons in the direction opposite to the [conventional] current. This cascade of electrons is what happens close to the speed of light, not the electron movement itself.

1. The **signal of electrical current (that is electromagnetic radiation) travels anywhere between about 50-99% the speed of light** (dependent on a number of conditions) depending upon the material through which it travels (based on a dielectric behavior known as permittivity)
2. The **drift velocity of electrons** within a copper wire is $25 \mu\text{m/s}$, so how does anything ever turn on?
3. The **hose effect** - The electrons at the light switch will almost certainly never pass through a light bulb, but they will move around and bump into their neighbors which bump into their neighbors which bump into their neighbors, etc., until it causes the electrons nearest the light to pass through. This is how water at a spigot is able to push water at the end of a hose.
4. **How current and drift velocity related?** - Mathematically, it's represented as follow:

$$I = \frac{Q}{t} = \frac{neAd}{d/v_d} \quad (1.3)$$

Imagine there is a cylindrical wire with length d and cross-sectional area A . Suppose there are n electrons per unit volume and each with a charge of e . Then in the whole cylindrical wire, the total charge is derived by multiplying the total volume Ad , the number of electron per unit volume n , and the elementary charge e . This is the numerator part of the story. On the denominator is the time component. Assume all electrons are moving in one direction and with drift velocity. It would take t amount of time for the last electron to move a distance of d from one end to the other and exit the cylindrical wire. In fact, this is how we, in a microscopic sense, perceive the concept of current, which is defined by the total charge that passes through a single reference cross-section over a given amount of time.

1.4 Potential (difference)

1. The amount of work needed to move a unit of (positive) charge from a reference point to another point [without producing an acceleration]).

2. Potential is measured in “volts” and is often called “voltage”. In this class we will endeavor to avoid such a term as it can be very confusing to talk about potential as if there were such a *thing* as voltage.
3. Defined as

$$v := \frac{dw}{dq} \quad (1.4)$$

4. Potential describes the *potential* to do something. Increasing the potential is akin to increasing the height of a cliff. The height does not *do* anything other than increase what can be done on the drop. If potential is the cliff’s height, charge would be pebbles you’d drop off the side, and current describes how fast those pebbles fall.
5. In this class, and for the vast vast majority of electrical engineering work, we care about the *difference* in potential. One element held at 100 billion volts and another held at 100 billion + 1 volts has a *potential difference* of 1 V, which is less than a single AA battery.
6. Voltage can also be thought of as how badly the current “wants” to flow, while current is the actual flow of charges per second. Since charge flows but not the voltage, voltage can exist without current - a single charge induces a voltage. On the other hand, current can’t exist without voltage since having a current means that charges are flowing, and if charges are flowing there is a potential difference across the charges.
7. Some typical voltages to be aware of

Consumer level batteries (AA, AAA): 1.5 V (DC); 9 V (DC)

Car batteries: 12 V (DC)

The “mains” (levels provided by power companies to consumers): 110-120 V (AC) and 220-240 V (AC) in America

Power transmission lines: 110-1200 kV (AC), transformers are used to step up and down the potential before used by consumers

1.5 Power

1. The time rate of expending or absorbing energy.
2. Quantifies the rate of energy transfer.

3. Mathematically:

$$p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = v \cdot i \quad (1.5)$$

4. Measured in watts: $1 \text{ W} = 1 \frac{\text{J}}{\text{s}} = 1 \frac{\text{N} \cdot \text{m}}{\text{s}} = 1 \frac{\text{kg} \cdot \text{m}^2}{\text{s}^3} = 1 \text{ V} \cdot 1 \text{ A}$
5. **Passive sign convention:** If current enters through the positive terminal of an element, $p = +vi$; if current enters through the negative terminal of an element, $p = -vi$.

1.6 Energy

1. The capacity to do work.
2. Measured in joules.
3. $E = \int \frac{dw}{dt} dt \rightarrow \text{power} \times \text{time}$
4. $\text{J} = \frac{\text{kg} \cdot \text{m}^2}{\text{s}^2} = \text{N} \cdot \text{m} = \text{Pa} \cdot \text{m}^3 = \text{W} \cdot \text{s} = \text{C} \cdot \text{V}$

1.7 Conservation

Here, as elsewhere, things will be conserved. In electrical circuits there are two laws of conservation that will matter most for us:

1. **The Conservation of Mass.** The conservation of mass means that no mass can be added to or removed from a circuit without being accounted for. Put differently, in a closed system (the type we will concern ourselves with here) no mass is added or removed.

In electrical circuits, the mass we care the most about are the charges whipping around. Thus, for us, *the amount of charge within a circuit must remain constant.*

2. **The Conservation of Energy.** The conservation of energy means that no energy can be added to or removed from a circuit without being accounted for. Put differently, in a closed system (the type we will concern ourselves with here) no energy is added or removed.

In electrical circuits, the energy we care the most about is the potential provided by sources and depleted by other elements in the circuits. Thus, for us, *the sum of potentials within a circuit must equal zero.*

In evaluating circuits, the main focus of the first third of this class, it will be the application of these two conservative laws that will enable us to “solve” them. That is, by understanding (1) how energy is generated and used and (2) how charges move around in closed loops (“circuits”) we will be able to predict the behavior of the myriad electrical systems which may cross our paths.

1.8 Worksheet

1.8.1 Problem 1, constant charge through a cross-section

How much charge passes through a cross-section of a conductor in 60 seconds if a DC current value is measured at 0.1 mA? **Solution**

1.8.2 Problem 2, arbitrary charge through a cross-section

Determine the total charge entering a terminal between $t = 0$ seconds and $t = 10$ seconds if the current (in amps) passing through is

$$i(t) = \frac{1}{\sqrt{5t + 2}}. \quad (1.6)$$

Solution

1.8.3 Problem 3, a "tera"ble puzzle

Approximately how much current is necessary to transmit one terabyte of information in an hour? **Solution**

1.8.4 Problem 4, power necessary to run a pacemaker

A cardiac pacemaker will provide approximately 5,000 J of energy over 5 years. Determine the capacity of a 5 V lithium battery necessary to drive this pacing such that only 40% of its energy is spent over that time. **Solution**

1.8.5 Problem 5, energy needed to excite a neuron

A colleague of yours has been in their lab ginning up new neurons. You, as their resident electrical expert, are tasked with determining the energy consumed by the cell. If the current and voltage variations are found to be functions of time ($t \geq 0$)

$$i(t) = 3t \quad (1.7)$$

$$v(t) = 10e^{6t} \quad (1.8)$$

determine the energy consumed between 0 and 2 ms. **Solution**

1.8.6 Problem 6, a thump to the chest

- (a) A typical defibrillator delivers 200-1000 V in less than 10 ms. How much current is needed to deliver 120, 240, and 360 Joules?
- (b) A human heart weighs about 300 grams. From approximately how high of a cliff would one have to drop a heart such that the impact was equivalent to the energy delivered to someone's chest from a defibrillator? **Solution**

Chapter 2

An introduction: II. Circuit elements

Contents

2.1	Active v. passive	11
2.2	Ohm's Law and what it means	11
2.3	Sources	12
2.4	Resistors	12
2.4.1	Resistance, R	12
2.4.2	Resistivity, ρ	13
2.4.3	Conductance	13
2.5	Capacitors	14
2.5.1	Its time varying behavior	14
2.5.2	Charge accumulation	15
2.5.3	A simple example	15
2.6	Inductors	15
2.7	Impedance	16
2.7.1	A quick note on “imaginary” numbers	17
2.8	Equivalent impedance	17
2.8.1	Impedances in general	18
2.8.2	Resistors	18
2.8.3	Capacitors	18
2.8.4	Delta-Wye (Δ -Y) transformations	19
2.8.5	A few examples	19
2.9	Grounds	20

2.10	Conductors	20
2.11	Operational amplifiers ("Op-amps")	20
2.12	Diodes	20
2.13	Switches	20
2.14	Transistors	21
2.15	Transformers	21
2.16	Worksheet	22
2.16.1	Problem 1, expressing power in ohms	22
2.16.2	Problem 2, a couple toaster based problems	22
2.16.3	Problem 3, currently conducting power	22
2.16.4	Problem 4, conductance of a sodium channel	22
2.16.5	Problem 5, resistance of a simple tissue	22

01/15/2019

2.1 Active v. passive

1. Active elements are capable of generating energy while passive components cannot
2. **Active:** generators, batteries, operational amplifiers, "sources"
3. **Passive:** resistors, capacitors, inductors, i.e., most circuit elements

2.2 Ohm's Law and what it means

Ohm's Law is concerned with the relationship between voltage, or potential difference, and current across a conductor. The potential difference across a conductor is proportional to the current flowing through the conductor with the proportionality constant being denoted as R , or resistance. This can be expressed as:

$$V := iR \quad (2.1)$$

This essentially states that the drop in potential across the conductor, or resistor, is equivalent to the current flowing through the conductor and its resistance. When considering impedance, the equation can be modified to state:

$$V := iZ \quad (2.2)$$

2.3 Sources

1. **An ideal independent source** is an active element that provides a specified value of potential or current, regardless of other circuit elements.

Batteries and power supplies may be approximated as ideal potential sources.

2. **An ideal dependent (or controlled) source** is an active element in which the source quantity is controlled by another quantity (such as potential, current, temperature, measured resistance, etc.).
3. **An ideal potential source** will produce any current required to ensure that the terminal voltage stated is satisfied.
4. **An ideal current source** will produce any voltage required to ensure that the terminal current as stated is satisfied

5. Symbols

Voltage-controlled voltage source, VCVS

Current-controlled voltage source, CCVS

Voltage-controlled current source, VCCS

Current-controlled current source, CCCS

2.4 Resistors

Resistors are electrical (circuit) elements that resist the flow of electric charge (current); passive two-terminal components that implement a defined/“constant” resistance; meant to reduce current flow and change potential

2.4.1 Resistance, R

1. **Resistance** is the physical property describing an element’s ability to resist current and is most often represented by R
2. Resistance is measured in “ohms”, Ω , which is equivalent to 1 V/A
3. Resistance is one half of a broader physical phenomenon known as “**impedance**” - the property describing an element’s ability to *impede*

current. Impedance is typically represented by Z , which we'll explore more thorough in a bit.

2.4.2 Resistivity, ρ

1. The resistance of an element (such as a resistor) depends on three things:

Resistivity, ρ , of the material comprising the element, which is the *material's* ability to resist the flow of charges; measured in ohm-meters

Length, l , of the element; measured in meters

Area, A , of the cross-section of the element; measured in m^2

Such that $R = \rho \frac{l}{A}$

What units are we left with?

What are the effects of length and area?

2. **Materials with low resistivity** are generally called (and treated as) “conductors” as they are able to more effectively *conduct* the motion of electrical charges than materials with high resistivity
3. **Materials with very high resistivity** are generally used as “insulators” as they prevent the flow of current through them and thus *insulate* the current within prescribed bounds, such as with a copper wire with plastic wrapped around it.

Here is a link to a video that further explains the concepts of resistivity and resistance: <https://www.youtube.com/watch?v=4rsswT_Rv1M>.

2.4.3 Conductance

1. The inverse of resistance is conductance, G , which describes the ability of an element to conduct current
2. Measured in Siemens
3. Allows us express Ohm's law slightly differently, $i = Gv$, which says that the current generated through an element by a potential is directly proportional to some constant, namely conductance.
4. The material specific property **conductivity**, σ is measured in S/m

2.5 Capacitors

1. Passive two-terminal components that store energy in an electric field; introduces capacitance to a circuit.
2. Can be thought of as two conductive plates sandwiching a “dielectric” material. Essentially it is two “conductors” separated by a “non-conductive region”.
3. When a capacitor is attached across a source, an electric field develops across the dielectric causing a net positive charge to collect on one conductor and a net negative charge to collect on the other.
4. We can define the capacitance of an element mathematically as

$$C = Q/V \quad (2.3)$$

where C is capacitance in farads, Q is positive or negative charge on each conductor, and V is the potential between them

5. We can also represent capacitance by the voltage-based rate of charge accumulation: $C = dQ/dV$.

2.5.1 Its time varying behavior

Unlike resistors, capacitors have a *time-varying* element to that. That is, since $C = Q/V$, $V = Q/C$.

If we then recall Equation 1.2, we can write the time-dependent potential relationship of a capacitor

$$V(t) = \frac{Q(t)}{C} = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + V(t_0) \quad (2.4)$$

We can also recall¹ Equation 1.1, and represent the time-dependent current relationship as

$$I(t) = \frac{dQ(t)}{dt} = C \frac{dV(t)}{dt} \quad (2.5)$$

¹We could also take the derivative of the equation preceding this one and do a little rearrangement. As it turns out, these physical relationships are rather codified and thus can be gotten out by any number of means.

2.5.2 Charge accumulation

1. While charges accumulate on a capacitor, no current flows *through* the capacitor.
2. **Well, then why use them? After awhile won't the current just stop?** Yes, indeed it will – in a DC circuit!
3. The capacitor will become “charged” over time, eventually reaching the same potential as that established across it, e.g., by a source. Since potential only ever travels down potential gradients, if the capacitor and the source (say, a battery) are at the same potential, no current will flow.
4. Thus, a fully charged capacitor will act as an “open” circuit, while an uncharged capacitor will act as a “short” circuit.

2.5.3 A simple example

If we consider Ohm's law for a simple RC circuit (one in which a source, a resistor, and a capacitor are in series), we can describe the system by

$$V_0 = v_R(t) + v_C(t) \quad (2.6)$$

$$V_0 = i(t)R + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau \quad (2.7)$$

Taking the derivative of both sides:

$$0 = R \frac{di(t)}{dt} + \frac{1}{C} i(t) \quad (2.8)$$

$$0 = RC \frac{di(t)}{dt} + i(t) \quad (2.9)$$

$$i(t) = \frac{V_0}{R} \cdot e^{-t/RC} \quad (2.10)$$

$$v(t) = V_0 \left(1 - e^{-t/RC} \right) \quad (2.11)$$

$$Q(t) = C \cdot V_0 \left(1 - e^{-t/RC} \right) \quad (2.12)$$

2.6 Inductors

1. Passive two-terminal components that store energy in a magnetic field

2. Can be thought of as an insulated wire wound into a coil around a core (which may either be filled with a material or left open to the environment)
3. Behavior can be modeled as $L = \frac{\Phi}{I}$, where L is the inductance, Φ is the magnetic flux generated by a current, I .
4. By Faraday's law of induction, voltage induced by a change in magnetic flux through a circuit is

$$v = \frac{d\Phi}{dt} \quad (2.13)$$

which we can rewrite as

$$v = \frac{d}{dt}(Li) = L \frac{di}{dt} \quad (2.14)$$

5. In this class, at this level, and for most biomedical applications you're liable to experience in your tenure, you will not work extensively with inductors. However, you should be able to recall at least this much at a moment's notice to be able to ascertain a system's behavior.

2.7 Impedance

1. The measure of opposition a circuit element presents to a current when a potential is applied. (It is measured in ohms.)
2. It is "complex" in two sense of the term. First, the actual phenomenon itself comprises complex numbers; that is, there is both a "real" and an "imaginary" component.

The real component is known as resistance, R

The imaginary component is known as reactance, X

Impedance can be represented as a combination of either

Resistance and reactance: $\mathbf{Z} = R + jX$, where \mathbf{Z} is impedance, R is resistance, and X is reactance, or

Magnitude and phase: $\mathbf{Z} = |Z|e^{j\theta}$, where $|Z|$ is the magnitude of the impedance vector, \mathbf{Z} , and θ is the phase of said vector (i.e., the delay between current and potential). Phase, θ is equivalent to $\tan^{-1}(X/R)$

3. Impedance is also complex in the sense that it is complicated. The impedance of an object is a factor of many parameters including permittivity, geometry, quantum states, thermal stability, etc. Let us not view this sort of complexity as an impediment to our understanding of impedance.
4. The inverse of impedance is **admittance**, Y , and comprises a real component, **conductance**, G , (which is the inverse of resistance) and an imaginary component, **susceptance**, B (which is the inverse of reactance). (It is measured in Siemens.)

$$Y = G + jB$$

2.7.1 A quick note on “imaginary” numbers

The term “imaginary” is an unfortunate name for an excellent mathematical tool. All the imaginary operator – in this class represented by $j = \sqrt{-1}$ – is a type of number “orthogonal” to our “real” numbers. Imaginary numbers are no less “real” than real numbers. Unfortunately, they aren’t necessarily the most intuitive to our little mammalian brains and thus we must be trained to work with them. However, as we will see in this class, they can be quite useful.

2.8 Equivalent impedance

1. It will often be more convenient to think about the impedance which a component burdens a system with (or the conductance which it affords) rather than its resistance. **Therefore, we need to begin to think in terms of equivalent impedances as we start to evaluate circuits.**
2. Recall Ohm’s law

$$\text{Resistors, } v = iR \quad \rightarrow Z_{eq,R} = R$$

$$\text{Capacitors, } v = \frac{1}{C} \int i dt \quad \rightarrow Z_{eq,C} = \frac{1}{j\omega C}$$

$$\text{Inductors, } v = L \frac{di}{dt} \quad \rightarrow j\omega L$$

I want to plant a flag here for you to notice the relationship between the $j\omega$ terms from the capacitor and inductor and the corresponding derivative and integral forms of current in the Ohm’s law representation. This will become very important once we get into the Laplace and Fourier transforms.

3. We must also recognize that few will be the circuits comprising but a single element. As such, we should know how to find the equivalent impedance of many elements.

2.8.1 Impedances in general

Series

$$Z_{eq,series} = Z_1 + Z_2 + Z_3 + \dots \quad (2.15)$$

Parallel

$$\frac{1}{Z_{eq,parallel}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots \quad (2.16)$$

A special case to remember. When dealing with only two elements:

$$Z_{eq} = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2} \quad (2.17)$$

2.8.2 Resistors

Series

$$R_{eq,series} = R_1 + R_2 + R_3 + \dots \quad (2.18)$$

Parallel

$$\frac{1}{R_{eq,parallel}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \quad (2.19)$$

2.8.3 Capacitors

Series

$$\frac{1}{C_{eq,series}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots \quad (2.20)$$

Parallel

$$C_{eq,parallel} = C_1 + C_2 + C_3 + \dots \quad (2.21)$$

2.8.4 Delta-Wye (Δ -Y) transformations

Going from Delta to Wye

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c} \quad (2.22)$$

$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c} \quad (2.23)$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c} \quad (2.24)$$

Going from Wye to Delta

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_1} \quad (2.25)$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_2} \quad (2.26)$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_3} \quad (2.27)$$

$$(2.28)$$

2.8.5 A few examples

Example 1 Find the equivalent resistance, if a resistor $R_1 = 10 \text{ k}\Omega$ is connected in parallel to $R_2 = 3.3 \text{ k}\Omega$.

$$\text{Solution. } R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2} = \frac{(10)(3.3)}{10 + 3.3} = 2.48 \text{ k}\Omega$$

Example 2 Find the equivalent resistance of three parallel-connected resistors of equal value. If $R = R_1 = R_2 = R_3 = 10 \text{ k}\Omega$, what's R_{eq} ?

Solution. Recall, Equation 2.19

$$\frac{1}{R_{eq}} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} \rightarrow 3R_{eq} = R \rightarrow R_{eq} = \frac{R}{3} \rightarrow R_{eq} = \frac{10k}{3} = 3.33k\Omega \quad (2.29)$$

Example 3 Four resistors are connected in parallel. $R_1 = 10 \text{ k}\Omega$, $R_2 = 1 \text{ k}\Omega$, $R_3 = 5 \text{ k}\Omega$, and $R_4 = 3 \text{ k}\Omega$. Calculate their equivalent resistance.

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \quad (2.30)$$

$$\frac{1}{R_{eq}} = \frac{1}{10k} + \frac{1}{1k} + \frac{1}{5k} + \frac{1}{3k} \quad (2.31)$$

$$= 612.3 \Omega \quad (2.32)$$

2.9 Grounds

1. A reference point in an electrical circuit from which potentials are measured
2. A common return path within a circuit

2.10 Conductors

1. Allow from the transmission of electrical energy
2. Serve to connect circuit elements
3. Also known as wires and traces
4. Within circuit schematics we must be mindful of “junctions” and “jumps” in conductors

2.11 Operational amplifiers (“Op-amps”)

1. Active components that deliver the amplified difference between its inverting and non-inverting terminals
2. Will be discussed at length in the next class and along with resistors, capacitors, and sources, will be among the primary circuit components we work with
3. Allow us to model mathematical functions; any mathematical function that can be represented by a differential equation can be replicated with an op-amp

2.12 Diodes

Two-terminal circuit elements that allow current to flow only in one direction

2.13 Switches

Make/break/change circuit paths (thereby diverting current or removing potential)

1. Single pole, single throw, SPST

2. Single pole, double throw, SPDT
3. Double pole, single throw, DPST
4. Double pole, double throw, DPDT

2.14 Transistors

2.15 Transformers

1. Transfer electrical energy between circuits using induction
2. Allows for the effective transmission of power and the stepping up/down of potential
3. Crucial for the transmission, distribution, and utilization of AC

2.16 Worksheet

2.16.1 Problem 1, expressing power in ohms

Utilizing Ohm's law, express units of power to include ohms.

Solution

2.16.2 Problem 2, a couple toaster based problems

A toaster draws 2 A at 120 V. What is its resistance?

Solution

How much current is drawn by a toaster with a resistance of $10\ \Omega$ at 110 V?

Solution

2.16.3 Problem 3, currently conducting power

In the circuit shown, calculate the current, i , the conductance, G , and the power, p .

Solution

2.16.4 Problem 4, conductance of a sodium channel

Conductance (G/A) of a sodium channel of a cell membrane at a specific time is $10\ \text{mS}/\text{cm}^2$. If the channel length as 100 nm, what is its conductivity?

Solution

2.16.5 Problem 5, resistance of a simple tissue

Determine the resistance of a homogenous and isotropic tissue with a cross-sectional area which can be described by the functions $y = 8 - x^2$ from $x = -2\ \text{cm}$ to $x = +2\ \text{cm}$, a length of 10 cm (parallel to the z-axis), and a resistivity of $80\ \Omega\text{m}$.

Solution

Chapter 3



An introduction: III. Operational amplifiers

01/17/2019

Contents

3.1	Some details	24
3.2	Some rules	25
3.3	Some conveniences	25
3.4	Some examples	26
3.4.1	Inverting amplifier	26
3.4.2	Non-inverting amplifier	27
3.4.3	Voltage follower	28
3.4.4	Summing amplifier	28
3.4.5	Differential amplifier (as homework)	28

3.1 Some details

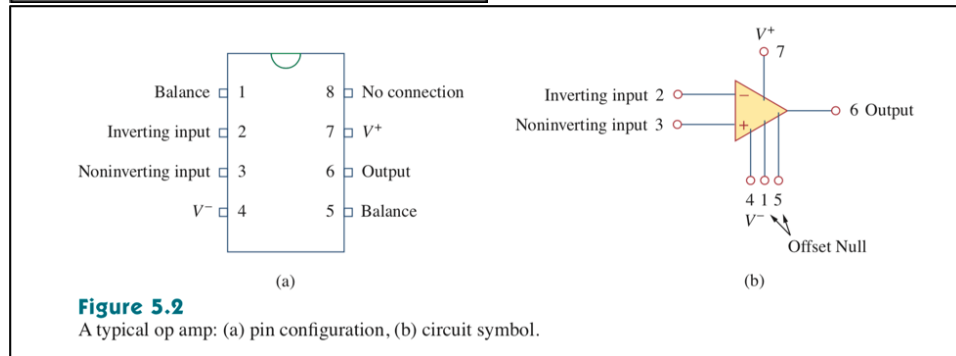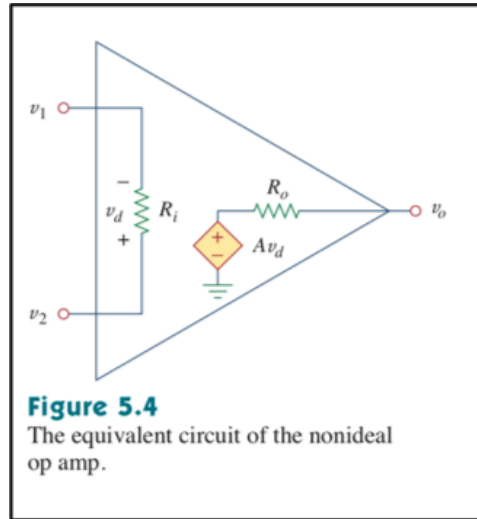

1. Behaves like a voltage-controlled voltage source
2. They can amplify, sum, subtract, multiply, differentiate, integrate
3. They are active circuit elements
4. Though they have somewhat more complicated internal workings, we typically represent them in electrical circuits as a triangle with three (sometimes five) very important terminals:

An inverting input ($-$ sign, typically represented up top for convenience, but it need not be)

A non-inverting input ($+$ sign, typically on bottom)

An output

3.2 Some rules

There are **three important features of ideal operational amplifiers** that we must understand thoroughly. These are things worth stamping in your brain.

1. **Infinite open-loop gain.** The “A” of the gain is infinitely large such that any difference in voltages V_1 and V_2 causes an enormously large output voltage. As much as is being supplied. (The real value of gain in most operational amplifiers is between 10^5 and 10^8 .)
2. **Infinite input impedance.** Current cannot travel between the inverting and non-inverting terminals. (Really, the impedance is between 10^5 and 10^{13} ohms and is often signal dependent.)
3. **Zero output impedance.** There is no loss transmitting a voltage difference to the output. (Really is about 10-100 ohms and is chip dependent.)

3.3 Some conveniences


1. With infinite input impedance, no current can flow into or out of the terminals and hence i_1 and i_2 are equal to 0.
2. Since no current flows across the terminals, the terminals are at equal potential. Hence “ $v_1 = v_2$ ”.

Some extra facts with operational amplifiers are that they can be combined with a capacitors to create different filters. Adding a capacitor in series with the input resistor creates a ”high-pass filter” amplifier, where it passes signals with frequency higher than a specific cutoff frequency and attenuates signals lower than the cutoff. Adding a capacitor in parallel with the feedback resistor creates a ”low-pass filter” amplifier, where it passes signals with frequency lower than the cutoff and attenuates signals higher than it. The corner frequency for the cutoff may be calculated with $f=1/(2\pi RC)$. Having both capacitors would create a band-pass filter which attenuates signals lower than the lower cutoff and higher than the upper cutoff frequencies.

3.4 Some examples

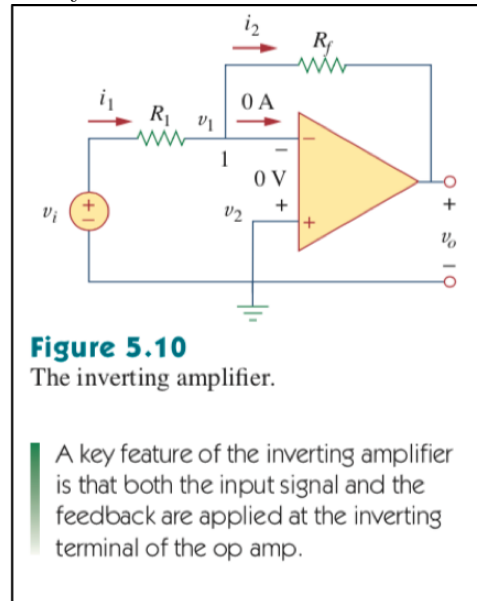3.4.1 Inverting amplifier

We will apply the conservation of mass at this point to solve our equations. This is among the simplest and most effective ways to add gain to a circuit. So much so that you will use it again and again and again in life and especially in labs




We apply KCL at the node for v_1

1. $i_1 - i_2 - i_3 = 0$
2. $i_3 = 0$
3. $i_1 - i_2 = 0$
4. $i_1 = i_2$
5. $i_1 = (v_i - v_1)/R_1$
6. $i_2 = (v_1 - v_o)/R_f$
7. $(v_i - v_1)/R_1 = (v_1 - v_o)/R_f$
8. $v_1 = v_2 = 0$
9. $v_i/R_1 = -v_o/R_f$

10. $V_o = -R_f/R_1 * V_i$

11. R_2/R_1 is our gain, gain factor.

3.4.2 Non-inverting amplifier

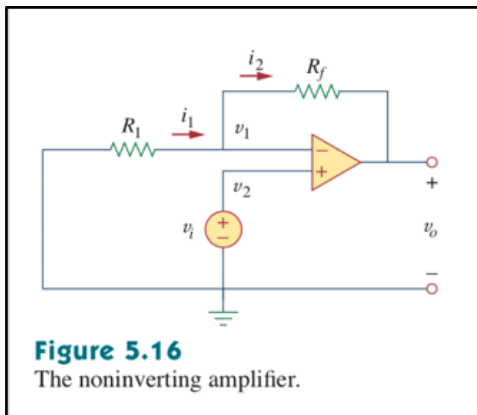

Again, the name might imply what it does. It will amplify our input signal without inverting it.

We can again perform Nodal analysis.

1. $I_1 - i_2 - i_3 = 0$

2. $I_3 = 0$, since no current enters the non-inverting input


3. $I_1 = i_2$

4. $(V_g - v_2)/R_1 = (v_2 - V_o)/R_f$

5. $v_2/R_1 = (v_i - V_o)/R_f$

6. $V_o = (1 + R_f/R_1) * V_i$

3.4.3 Voltage follower

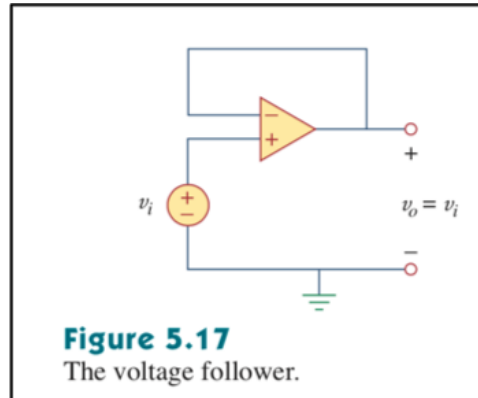

What if we didnt have any resistors? $\rightarrow V_i = v_2 = v_1 = V_o \rightarrow V_i = V_o$

3.4.4 Summing amplifier

3.4.5 Differential amplifier (as homework)

Chapter 4

Circuit analysis: I. Nodal analysis

01/22/2019

Contents

4.1	Nodes and branches	30
4.1.1	The Seven Bridges of Königsberg	30
4.1.2	Independence	31
4.1.3	Fundamental theorem of network topology	31
4.2	Kirchhoff's Laws	32
4.2.1	Kirchhoff's Current Law	32
4.2.2	Kirchhoff's Voltage Law	33
4.2.3	A few examples	33
4.3	Nodal analysis	36
4.3.1	The procedure	36
4.4	Solving simultaneous equations	37
4.4.1	Cramer's Rule	37
4.5	Worksheet	40
4.5.1	Problem 1, KCL at a few nodes	40
4.5.2	Problem 2, matrix notation	40
4.5.3	Problem 3, Cramer's rule	40
4.5.4	Problem 4, Straight to the matrix	40

4.1 Nodes and branches

1. **A branch** is any two-terminal element. (examples: Resistor, Capacitor, Wire, etc.)

*A **branch** is any two-terminal element. What are some two-terminal elements we've learned?*

2. **A node** (junction) is a point of connection between two or more branches.

*A **node** is a point of connection between two or more branches. Often indicated by a dot. What else have we called a node? A junction.*

3. A loop is **independent** if at least one branch is not part of any other independent loop.

*A **loop** is any closed path within a circuit. A closed path formed by starting at a node, passing through a set of nodes, returning to the starting node without passing through any node more than once.*

4.1.1 The Seven Bridges of Königsberg

The Königsberg bridge problem asks if the seven bridges of the city of Königsberg (left figure; Kraitchik 1942), formerly in Germany but now known as Kaliningrad and part of Russia, over the river Pregel can all be traversed in a single trip without doubling back, with the additional requirement that the trip ends in the same place it began.

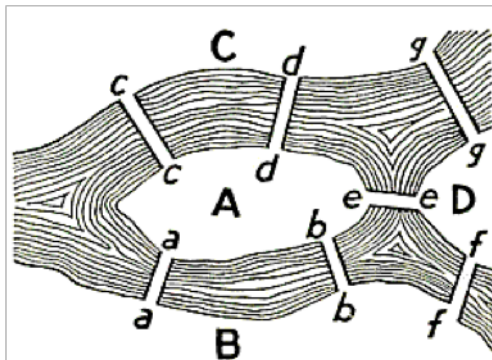


FIGURE 98. *Geographic Map:
The Königsberg Bridges.*

4.1.2 Independence

A loop is independent if it contains at least one branch which is not a part of any other independent loop

1. Each of the loops in the circuit at right are independent
2. Independent loops lend themselves to sets of equations to be solved!

4.1.3 Fundamental theorem of network topology

Fundamental theorem of network topology states that the number of branches, b , must equal the sum of the independent loops, l and nodes, n minus one, that is

$$b = l + n - 1 \quad (4.1)$$

With this fundamental theorem we can also redefine/refine our definition of series and parallel.

- **Series** — two or more elements share a single node and thereby carry the same current
- **Parallel** — connected to the same two nodes and thereby have the same voltage across them (potential difference)

How many branches and nodes does the circuit in Fig. 2.14 have? Identify the elements that are in series and in parallel.

Practice Problem 2.4

Answer: Five branches and three nodes are identified in Fig. 2.15. The 1- Ω and 2- Ω resistors are in parallel. The 4- Ω resistor and 10-V source are also in parallel.

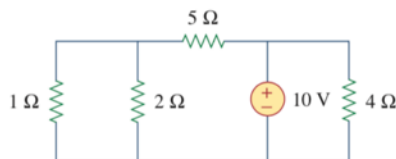


Figure 2.14
For Practice Prob. 2.4.

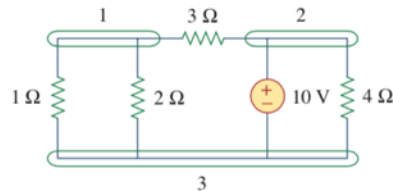


Figure 2.15
Answer for Practice Prob. 2.4.

4.2 Kirchhoff's Laws

I am not personally a fan named laws of nature, especially ones which are mere recapitulations of already perfectly good laws. Thus do we introduce Kirchhoffs laws, known as

- Kirchhoffs current law (“KCL”)
- Kirchhoffs voltage law (“KVL”)

These are, as far as Im concerned, mere restatements of *the conservation of mass* and *the conservation of energy*, respectively.

4.2.1 Kirchhoff's Current Law

Kirchhoff's current law states that any node (junction) in an electrical circuit, the sum of currents flowing into that node is equal to the sum of currents flowing out of that node.

- Put differently, the algebraic sum of currents entering a node (or any closed boundary) is zero
- For those mathematically inclined among us, that is: $\sum_{x=1}^n i_x = 0$
- Another way this often gets stated is by saying that the algebraic sum of charges within a system cannot change and is thus sometimes referred to as “the conservation of charge”.
- Well since all of our charge carriers are merely particles (electrons, protons, ions, etc.), this is just another layer over the top of the underlying law which is that mass cannot be created or destroyed.
- However, Kirchhoff's formulation of this law (conserving charge, mass) is useful in circuits as it gives us a great tool, being able to say that current going in is equal to current going out
- For the figure $i_1 + (-i_2) + i_3 + i_4 + (-i_5) = 0 \rightarrow i_1 + i_3 + i_4 = i_2 + i_5$
- KCL forms the basis of a technique well spend the next couple of lectures on known as nodal analysis because we evaluate the current going into and coming out of nodes

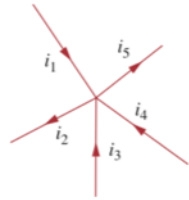


Figure 2.16
Currents at a node illustrating KCL.

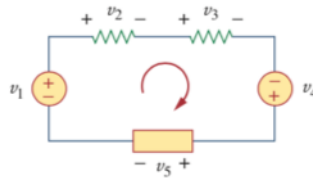


Figure 2.19
A single-loop circuit illustrating KVL.

4.2.2 Kirchhoff's Voltage Law

Kirchhoff's voltage law states that the sum of electrical potential differences (voltage) around any closed network is zero

- That is, for any closed path (loop), the sum of voltages is zero.
- Mathematically: $\sum_{m=1}^M v_m = 0$, where M is the number of voltage drops (caused by circuit elements) in the loop and v_m is the m th voltage drop
- The sum of voltage rises = the sum of voltage drops

$$v_1 + (-v_2) + (-v_3) + v_4 + (-v_5) = 0$$

$$v_1 + v_4 = v_2 + v_3 + v_5$$

4.2.3 A few examples

1. Simple 1 Vs 1 R circuit; $V_s = 10$, $R = 1 \text{ kohm}$, $I = 0.01 \text{ A} / 10 \text{ mA}$
2. Simple 1 Vs 2 R in series; $V_s = 10$, $R = 1 \text{ kohm}$, $I = 0.005 \text{ A} / 5 \text{ mA}$
What does KCL tell us? (Current is the same through resistors).

3. Simple 10 mA source, 2 R (1 kohm) in parallel; What is the voltage?

$$i_1 + (-i_2) + (-i_3) = 0 \rightarrow i_1 = i_2 + i_3 \rightarrow i_1 = V/R_1 + V/R_2$$

$$0.01 = V/1000 + V/1000 \rightarrow 0.01 = 2V/1000 \rightarrow 0.010/2 * 1000 = 5$$


V

Nodes are at the same voltage!

4. 10 mA up, 5 mA down, 2 R (1 kohm), Rl (500 ohm), all in parallel. What is the current through load Rl? [have someone come to the board and solve]

When current sources are in parallel they add together

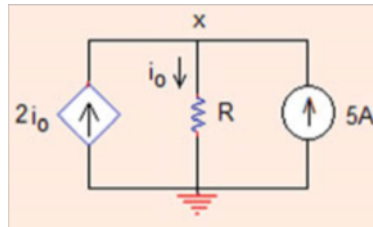5. For the circuit shown below, use KCL to find the remaining branch currents



2.13 For the circuit in Fig. 2.77, use KCL to find the branch currents I_1 to I_4 .

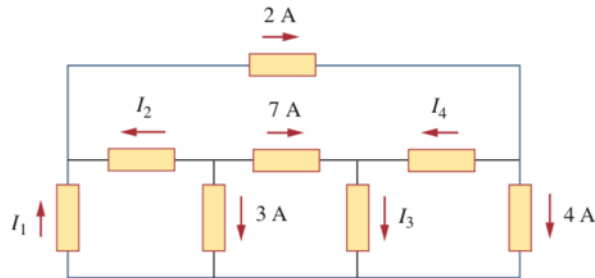


Figure 2.77
For Prob. 2.13.

For Figure 2.13, you know to use KCL because the circuit contains two current sources. Ideal current sources will deliver whatever potential is necessary to obtain the desired current so we don't know how potential behaves through it. If we look at node x and arbitrarily set i_1 as entering the node from the left, i_2 as exiting the node down the branch containing the resistor, and i_3 as entering the node from the right, then:

$$i_1 - i_2 + i_3 = 0$$

$$2i_0 - i_0 + 5 = 0$$

$i_0 = -5A$ The negative sign just means that the arbitrary direction we chose for our analysis is opposite of the actual direction of current flow

For Figure 2.77, start at a node with only one unknown current such as the upper right node.

$$2 - i_4 - 4 = 0$$

$$i_4 = -2A \text{ Repeat the process for remaining nodes}$$

$$7 + i_4 - i_3 = 0$$

$$i_3 = 7 + (-2) = 5A$$

$$-i_2 - 3 - 7 = 0$$

$$i_2 = -10A$$

$$i_1 + i_2 - 2 = 0$$

$$i_1 = 2 - (-10) = 12A$$

We could check our work by performing nodal analysis at the last node. However, it is not a necessary step as we have already found the desired unknowns.

4.3 Nodal analysis

Nodal analysis — a general circuit analysis technique in which we try to determine the potential difference between nodes by applying KCL and KVL (in my experience, usually focusing a bit more on KCL)

Your textbook offers the following description of the technique which seems pretty good to me:

1. Select a node as a reference. Assign voltages (v_1, v_2, \dots, v_{n-1}) for the remaining $n-1$ nodes, all of which will be referenced with respect to the reference node.
2. Apply KCL to each of the $n-1$ nonreference nodes. Use Ohms law to express the branch currents in terms of node voltages.
3. Solve the resulting simultaneous equations (system of equations) for each unknown node voltage.
4. It's as easy as that! But, well, actually, it can get a little hairy once you start to apply it in earnest.

4.3.1 The procedure

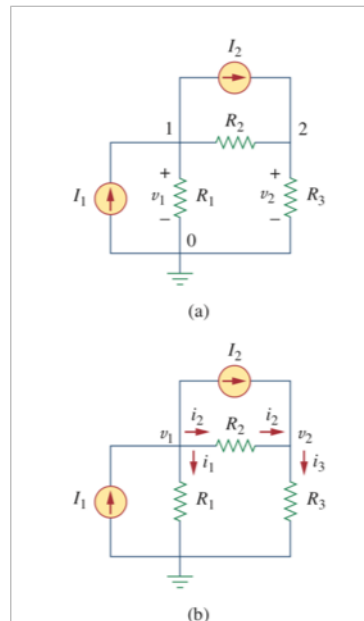


Figure 3.2

Typical circuit for nodal analysis.

1. Begin by putting a reference, usually a “ground”

This ground can be one of two sorts: (1) **Earth ground** in which ultimately the whole earth is used as the reference point; or **Chassis ground** in which the case of the device in which the circuit is in will act as a reference as it will presumably be sufficiently large as to serve fine [this is also partly the reason why you can “feel” a MacBook charge up its charger does not utilize a traditional “earth ground”

Either will suffice for our purposes here

2. Next we label all the nodes.

How many branches, nodes, and loops?

5 branches, 3 nodes, 3 loops. Satisfies our network condition.

You can give them any label you want, but I find working your way up from the ground in a clockwise manner and numbering them sequentially is a good habit to get into.

Keep in mind that we typically set our reference node to have a voltage of 0. We can actually set it to be anything we like, but the math is often easier if we just make it 0.

3. Then we apply KCL to each nonreference node in the circuit.

At node 1, $IA - i1 - i2 - IB \rightarrow IA = IB + i1 + i2$

At node 2, $IB + i2 - i3 \rightarrow IB + i2 = i3$

Once we've got that, now it's a matter of applying Ohm's law. Though typically written as $V = iR$, it is perhaps more helpful to write its full extension here and note that $(V_a - V_b) = iR$

$$I = (V_a - V_b)/R$$

Thus we can state

$$I1 = (v1 - v0)/R1 \rightarrow I1 = G1(v1 - v0)$$

$$I2 = (v1 - v2)/R2 \rightarrow I2 = G2(v1 - v2)$$

4.4 Solving simultaneous equations

4.4.1 Cramer's Rule

When given a system of linear equations, Cramer's Rule allows us to solve directly for the specific variable whose value we are looking for.

To use Cramer's Rule, the system of equations must satisfy two conditions:

1. There must be the same number of equations as variables (the coefficient matrix must be a square).
2. The determinant of the coefficient must be non-zero.

Use the following steps to apply Cramer's Rule:

1. Write the coefficient matrix of the system (call this matrix A). Make sure this is a square matrix; otherwise Cramer's Rule is not applicable.
2. Compute the determinant of matrix A. Make sure that this value is non-zero; otherwise Cramer's Rule is not applicable here.
3. Suppose the first variable of the system is x. Write the matrix Ax by placing the column of numbers to the right of the equals sign as the first column of Ax and using the non-x coefficients of matrix A as the remaining columns.
4. The value of x is the determinant of Ax divided by the determinant of A.
5. Repeat steps 3 and 4 to solve for any other variable as needed.

Example implementing Cramer's Rule: We will use the following system of equations to demonstrate how to use Cramer's Rule to solve for the value of x:

$$x + y + z = 4 \quad -x + 2y = 1 \quad -y + z = 1$$

1. Write the coefficient matrix A and check that it is a square matrix:

$$A = \begin{bmatrix} 1 & 1 & 1 \\ -1 & 2 & 0 \\ 0 & -1 & 1 \end{bmatrix}$$

2. Solve for the determinant of A. ($\det A = 4$). The determinant does not equal zero.
3. Write the matrix Ax:

$$Ax = \begin{bmatrix} 4 & 1 & 1 \\ 1 & 2 & 0 \\ 1 & -1 & 1 \end{bmatrix}$$

4. Solve for the determinant of Ax . ($-\det A = 4$).
5. Solve for the value of x :


$$x = \frac{|\det Ax|}{|\det A|} x = 1$$

Reference: Explanation and example inspired by "Solving System of Linear Equations: (lesson 4 of 5), Cramers Rule", MathPortal: <https://www.mathportal.org/algebra/solving-system-of-linear-equations/cramers-rule.php>. [Accessed 23 January, 2019].

4.5 Worksheet

4.5.1 Problem 1, KCL at a few nodes

Use KCL to write equations at each node.

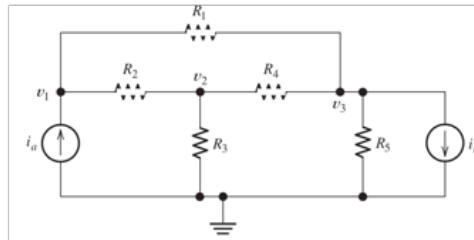

Solution

4.5.2 Problem 2, matrix notation

Write the matrix form of the equations written above.

Solution


4.5.3 Problem 3, Cramer's rule

Using Cramer's rule on the matrix equations above, what are the results?

Solution

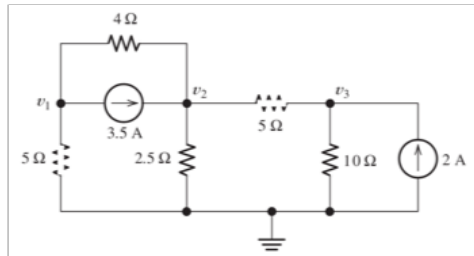4.5.4 Problem 4, Straight to the matrix

Write the node-voltage equations to the circuit at right in the matrix form.



Solution

Chapter 5

Circuit analysis: II. Mesh analysis

01/24/2019


Contents

5.1	Clarifications on the homework	42
5.2	Mesh analysis	42
5.3	Steps of mesh analysis	42
5.3.1	Important condition for use	42
5.4	An example	43
5.5	Another example	44
5.5.1	Solving it one way	44
5.5.2	Solving it another	45
5.6	Yet another example	46
5.7	Writing mesh equations directly in matrix form	47

5.1 Clarifications on the homework

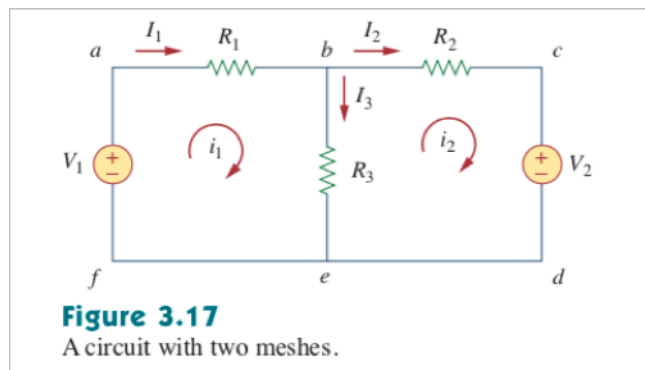5.2 Mesh analysis

- A mesh is a loop which does not contain any other loops within it.
- ABEF and BCDE are meshes. ABCDEF is not.
- We apply KVL to find the mesh currents within a given circuit (this can be particularly helpful / convenient when dealing with parallel circuits).



5.3 Steps of mesh analysis


1. **For each of your n meshes assign a mesh current (i_1, i_2, \dots, i_n).** You may draw them in any direction you want, but generally a nice clockwise direction will help with consistency.
2. **Apply KVL to each of the n meshes.** Use Ohms law to express the voltages in terms of the mesh currents
3. **Solve the resulting n simultaneous equations to get the mesh currents.**

5.3.1 Important condition for use

Unlike nodal analysis, mesh analysis only works for “planar networks” — that is one which can be written in two-dimensions without any branches.¹

¹Nonplanar networks can still be solved using nodal analysis.

5.4 An example

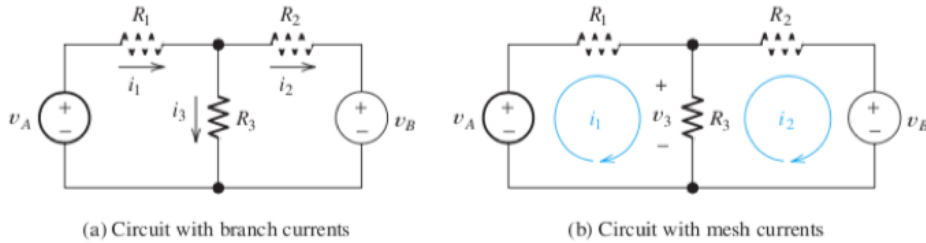

For the example seen above, we might at this point in our lives be tempted to solve the circuit with branch currents (the current that actually flows into and out of every branch. That is certainly a valid way by which to look at the problem. But now we’re going to try another. We’re going to try to understand “mesh currents”.

Those branch currents can be formed into a pair of coupled equations

$$V_A - R_1 i_1 - R_3 i_3 = 0 \quad (5.1)$$

$$V_B - R_2 i_2 - R_3 i_3 = 0 \quad (5.2)$$

We can also apply KCL at the node between the three resistors and recognize a third bounding equation: $i_1 + i_2 - i_3 = 0$. We can then solve these three equations through any number of means (substitution, elimination, etc.).

But mesh analysis allows us to model the situation more simply and often more efficiently.

We begin by defining two arbitrary mesh currents, i_1 and i_2 . Then we apply KVL as we do a “walk” around the loop defined by the mesh current.

$$V_A - R_1 i_1 - R_3(i_1 - i_2) = 0 \quad (5.3)$$

$$-R_3(-i_1 + i_2) - R_2 i_2 - V_B = 0 \quad (5.4)$$

This gives us two equations with two unknowns (the arbitrary mesh currents, i_1 and i_2 , we defined).

5.5 Another example

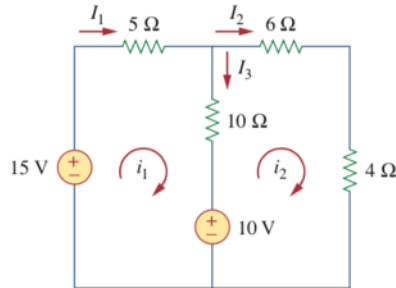


Figure 3.18
For Example 3.5.

For the circuit above, let's try to find the branch currents by performing mesh analysis (i.e., by first finding the mesh currents).

Solution.

Obtain mesh current using KVL. For mesh 1:

$$-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0 \quad (5.5)$$

which simplifies to

$$3i_1 - 2i_2 = 1 \quad (5.6)$$

For mesh 2:

$$6i_2 + 4i_2 + 10(i_2 - i_1) - 10 = 0 \quad (5.7)$$

simplifying to

$$i_1 = 2i_2 - 1 \quad (5.8)$$

5.5.1 Solving it one way

Perhaps the technique we'd most likely reach for if we knew nothing else about a situation is substitution. In this case, let's substitute equation 5.8 into equation 5.6:

$$6i_2 - 3 - 2i_2 = 1 \rightarrow i_2 = 1 \text{ A} \quad (5.9)$$

And plugging that result back in

$$i_1 = 2i_2 - 1 = 2 - 1 = 1 \text{ A} \quad (5.10)$$

And thus I_3 being equal to the difference in current between i_1 and i_2 is equal to zero.

5.5.2 Solving it another

Another way of doing this is by recognizing some of the techniques afforded to us by linear algebra. If we squint at the equations with a little bit of good brain wrinkling, we can see that

$$\begin{bmatrix} 3 & -2 \\ -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix} \quad (5.11)$$

is just as valid of way of putting it as any other.

In this form we can use a few techniques to solve for the unknowns. One technique to be aware of given its deployability in those times in which you might need to write out your work is *Cramer's rule*.

Cramer's rule says that

$$i_1 = \frac{\Delta_1}{\Delta} \quad (5.12)$$

$$i_2 = \frac{\Delta_2}{\Delta} \quad (5.13)$$

where

$$\Delta = \begin{vmatrix} 3 & -2 \\ -1 & 2 \end{vmatrix} = (3)(2) - (-1)(-2) = 4 \quad (5.14)$$

$$\Delta_1 = \begin{vmatrix} 1 & -2 \\ 1 & 2 \end{vmatrix} = (1)(2) - (1)(-2) = 4 \quad (5.15)$$

$$\Delta_2 = \begin{vmatrix} 3 & 1 \\ -1 & 1 \end{vmatrix} = (3)(1) - (-1)(1) = 4 \quad (5.16)$$

$$(5.17)$$

Thus

$$i_1 = \frac{4}{4} = 1 \quad (5.18)$$

$$i_2 = \frac{4}{4} = 1 \quad (5.19)$$

which agrees with the results we obtained before.

5.6 Yet another example

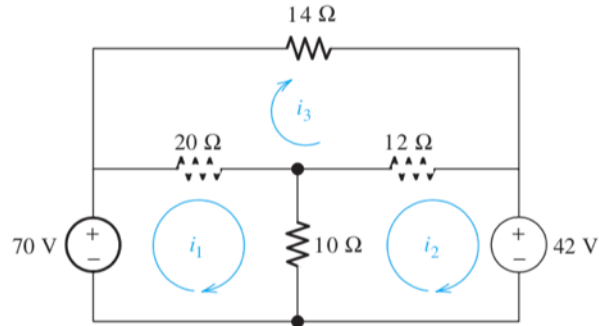


Figure 2.34 Circuit of Example 2.13.

Let's begin by defining the mesh currents (flowing clockwise around each mesh)

Mesh 1

$$20(i_1 - i_3) + 10(i_1 - i_2) - 70 = 0 \quad (5.20)$$

Mesh 2

$$10(i_2 - i_1) + 12(i_2 - i_3) + 42 = 0 \quad (5.21)$$

Mesh 3

$$20(i_3 - i_1) + 14i_3 + 12(i_3 - i_2) = 0 \quad (5.22)$$

Putting the equations into standard form:

$$30i_1 - 10i_2 - 20i_3 = 70 \quad (5.23)$$

$$-10i_2 + 22i_2 - 12i_3 = -42 \quad (5.24)$$

$$-20i_1 - 12i_2 + 46i_3 = 0 \quad (5.25)$$


In matrix notation that becomes:

$$\begin{bmatrix} 30 & -10 & -20 \\ -10 & 22 & -12 \\ -20 & -12 & 46 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 70 \\ -42 \\ 0 \end{bmatrix} \quad (5.26)$$

While this can be solved any number of ways, in MATLAB one can simply write $\mathbf{I} = \mathbf{R}/\mathbf{V}$, which should tell you something about what is “going on” mathematically in these operations.

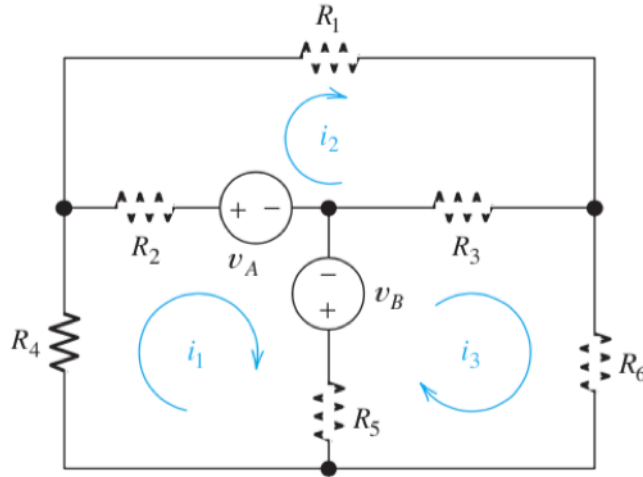5.7 Writing mesh equations directly in matrix form

Let's take a look at yet one more example.



We might, by now, begin to appreciate that one of our matrices is simply the resistances (impedances) of a mesh bundled up in one matrix, the currents bundled up in another, and the potentials bundled up in another, shown below.

$$\begin{bmatrix} r_{11} & r_{12} & r_{13} \\ r_{21} & r_{22} & r_{23} \\ r_{31} & r_{32} & r_{33} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} \quad (5.27)$$

To properly assemble these matrices there's just a few simple rules.

First, let's take a loop around each mesh and determine the equivalent impedance (of that mesh!)

- **Mesh 1.** $R_2 + R_5 + R_6$
- **Mesh 2.** $R_2 + R_1 + R_3$
- **Mesh 3.** $R_3 + R_6 + R_5$

These will comprise values along the diagonal of the resistance (impedance) matrix (r_{11} , r_{22} , and r_{33}).

Next, let's look for elements that are shared among meshes

- **Mesh 1 & 2** share R_2 , so r_{21} and r_{12} both become $-R_2$
- **Mesh 2 & 3** share R_3 , so r_{23} and r_{32} both become $-R_3$
- **Mesh 3 & 1** share R_5 , so r_{13} and r_{31} both become $-R_5$

Thus, our entire resistance matrix becomes

$$\begin{bmatrix} r_{11} & r_{12} & r_{13} \\ r_{21} & r_{22} & r_{23} \\ r_{31} & r_{32} & r_{33} \end{bmatrix} = \begin{bmatrix} (R_2 + R_5 + R_6) & -R_2 & -R_5 \\ -R_2 & (R_2 + R_1 + R_3) & -R_3 \\ -R_5 & -R_3 & (R_3 + R_6 + R_5) \end{bmatrix} \quad (5.28)$$

The matrix it butts up against is easy enough to construct, it is simply the mesh current of each mesh

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} \quad (5.29)$$

And the potential matrix is the sum of sources in the direction of the mesh current

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -v_A + v_B \\ v_A \\ -v_B \end{bmatrix} \quad (5.30)$$

Giving rise to a final form which can be solved efficiently by any computation engine we put before us.

$$\begin{bmatrix} (R_2 + R_5 + R_6) & -R_2 & -R_5 \\ -R_2 & (R_2 + R_1 + R_3) & -R_3 \\ -R_5 & -R_3 & (R_3 + R_6 + R_5) \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -v_A + v_B \\ v_A \\ -v_B \end{bmatrix} \quad (5.31)$$

Chapter 6

Circuit analysis: III. Supernodes and supermeshes

01/29/2019 Lecture 6.

Contents

6.1	A review of nodal and mesh analysis	50
6.1.1	Nodal analysis	50
6.2	Nodal analysis with an independent current source	51
6.3	A brief review of Cramer's rule	53
6.4	Nodal analysis with voltage sources, Supernodes	54
6.5	Nodal analysis with controlled sources	56
6.6	Mesh analysis with current sources	57
6.7	Mesh analysis with controlled sources, Super- meshes	57

6.1 A review of nodal and mesh analysis

6.1.1 Nodal analysis

1. Select a node as a reference. Assign voltages (v_1, v_2, \dots, v_{n-1}) for the remaining $n-1$ nodes, all of which will be referenced with respect to the reference node.
2. Apply KCL to each of the $n-1$ nonreference nodes. Use Ohms law to express the branch currents in terms of node voltages.
3. Solve the resulting simultaneous equations (system of equations) for each unknown node voltage.
4. (Its as easy as that! But, well, actually, it can get a little hairy once you start to apply it in earnest.)

6.2 Nodal analysis with an independent current source

Let's begin by analyzing the following circuit.

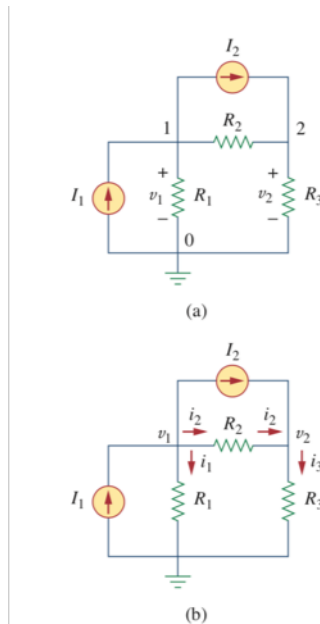


Figure 3.2
Typical circuit for nodal analysis.

1. Begin by putting a reference, usually a “ground”.
2. Next we label all the nodes.

How many branches, nodes, and loops? (5 branches, 3 nodes, 3 loops. Satisfies our network condition.)

You can give them any label you want, but I find working your way up from the ground in a clockwise manner and numbering them sequentially is a good habit to get into.

Keep in mind that we typically set our reference node to have a voltage of 0. We can actually set it to be anything we'd like, but the math is often easier if we just make it 0.

3. Then we apply KCL to each nonreference node in the circuit.

$$\text{At node 1, } I_A - i_1 - i_2 - I_B \rightarrow I_A = I_B + i_1 + i_2$$

At node 2, $IB + i2 - i3 - IB + i2 = i3$

Once weve got that, now its a matter of applying Ohms law. Thought typically written as $V = iR$, it is perhaps more helpful to write its full extension here and note that $(Va - Vb) = iR$

4. $I = (Va - Vb)/R$, Thus we can state

- $I1 = (v1 - v0)/R1 \rightarrow I1 = G1(v1 - v0)$
- $I2 = (v1 - v2)/R2 \rightarrow I2 = G2(v1 - v2)$
- $I3 = (v2 - v0)/R3 \rightarrow I3 = G3(v2 - v0)$

5. Now we can substitute these relationships into our previous equations

6.3 A brief review of Cramer's rule

system of equations	coefficient matrix's determinant	answer column	D_x : coefficient determinant with answer-column values in x -column
$2x + 1y + 1z = 3$ $1x - 1y - 1z = 0$ $1x + 2y + 1z = 0$	$D = \begin{vmatrix} 2 & 1 & 1 \\ 1 & -1 & -1 \\ 1 & 2 & 1 \end{vmatrix}$	$\begin{bmatrix} 3 \\ 0 \\ 0 \end{bmatrix}$	$D_x = \begin{vmatrix} 3 & 1 & 1 \\ 0 & -1 & -1 \\ 0 & 2 & 1 \end{vmatrix}$

Similarly, D_y and D_z would then be:

$$D_y = \begin{vmatrix} 2 & 3 & 1 \\ 1 & 0 & -1 \\ 1 & 0 & 1 \end{vmatrix} \quad D_z = \begin{vmatrix} 2 & 1 & 3 \\ 1 & -1 & 0 \\ 1 & 2 & 0 \end{vmatrix}$$

Evaluating each determinant, we get:

$$D = \begin{vmatrix} 2 & 1 & 1 \\ 1 & -1 & -1 \\ 1 & 2 & 1 \end{vmatrix} = (-2) + (-1) + (2) - (-1) - (-4) - (1) = 3$$

$$D_x = \begin{vmatrix} 3 & 1 & 1 \\ 0 & -1 & -1 \\ 0 & 2 & 1 \end{vmatrix} = (-3) + (0) + (0) - (0) - (-6) - (0) = -3 + 6 = 3$$

$$D_y = \begin{vmatrix} 2 & 3 & 1 \\ 1 & 0 & -1 \\ 1 & 0 & 1 \end{vmatrix} = (0) + (-3) + (0) - (0) - (0) - (3) = -3 - 3 = -6$$

$$D_z = \begin{vmatrix} 2 & 1 & 3 \\ 1 & -1 & 0 \\ 1 & 2 & 0 \end{vmatrix} = (0) + (0) + (6) - (-3) - (0) - (0) = 6 + 3 = 9$$


Cramer's Rule says that $x = D_x \div D$, $y = D_y \div D$, and $z = D_z \div D$. That is:

$$x = 3/3 = 1, \quad y = -6/3 = -2, \quad \text{and} \quad z = 9/3 = 3$$

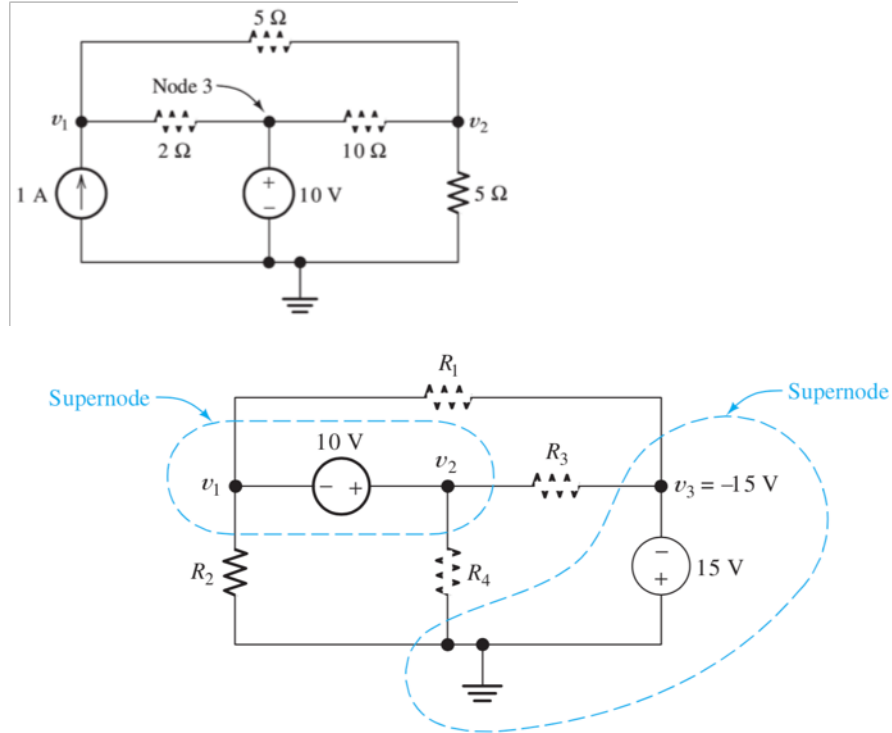6.4 Nodal analysis with voltage sources, Supernodes

We often pick the reference node at one end of the source (and then we have one less unknown node voltage to solve.

Typical examples can be typically solved. Write current equations at nodes 1 and two.



If we try to write a current equation at node 1, we must include a term for current through the 10V source. We could assign an unknown, or...

Or we can create a “supernode” which we do by drawing a dashed line around several nodes, including the elements between them, and apply KCL more broadly

- Recall that KCL says that the net current flowing through any closed surface must be equal to zero. Thus, we apply KCL to the supernode.

$$\frac{v_1}{R_2} + \frac{v_1 - (-15)}{R_1} + \frac{v_2}{R_4} + \frac{v_2 - (-15)}{R_3} = 0 \quad (6.1)$$

Now you might be tempted to write another current equation for the other supernode, however, you'd find that the equation is equivalent to the

6.4. NODAL ANALYSIS WITH VOLTAGE SOURCES, **SUPERNODES** 59


one we just found. If we tried to solve by substitution, all the terms would drop out and we'd see that the matrix was singular (the determinant is 0, it won't tell you anything new).

Instead we apply KVL, noting that $-v_1 - 10 + v_2 = 0$

Next, we find an expression for the controlling variable i_x in terms of the node voltages. Notice that since in this case i_x is the current flowing away from node 3 through R_3 , we can say $i_x = (v_3 - v_2)/R_3$.

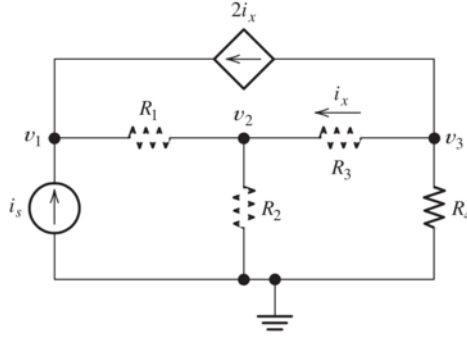6.5 Nodal analysis with controlled sources

We approach it the same way, but we're mindful of the dependence



Write KCL equations at each node, including the current of the controlled source, just as if it were an ordinary current source

$$\begin{aligned}\frac{v_1 - v_2}{R_1} &= i_s + 2i_x \\ \frac{v_2 - v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_2 - v_3}{R_3} &= 0 \\ \frac{v_3 - v_2}{R_3} + \frac{v_3}{R_4} + 2i_x &= 0\end{aligned}$$

Next, we find an expression for the controlling variable i_x in terms of the node voltages. Notice that since in this case i_x is the current flowing away from node 3 through R_3 , we can say $i_x = (v_3 - v_2)/R_3$.

$$\begin{aligned}\frac{v_1 - v_2}{R_1} &= i_s + 2\frac{v_3 - v_2}{R_3} \\ \frac{v_2 - v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_2 - v_3}{R_3} &= 0 \\ \frac{v_3 - v_2}{R_3} + \frac{v_3}{R_4} + 2\frac{v_3 - v_2}{R_3} &= 0\end{aligned}$$

So long as only three of those variable are unknown (say the voltages), then it can be solved by whatever method youd like.

6.6 Mesh analysis with current sources

6.7 Mesh analysis with controlled sources, Super-meshes

Chapter 7

Circuit analysis: IV. Circuit theorems

02/05/2019 Lecture 7.

Contents

7.1	Circuit theorems	60
7.2	Linearity	60
7.3	Superposition	61
7.4	Source transformation	63
7.5	Thevenin equivalents	63
7.5.1	An example	65
7.6	Norton equivalents	66
7.6.1	An example	66
7.7	Equivalents with dependents	68
7.8	A step-by-step procedure	69

7.1 Circuit theorems

Circuit theorems are ways of quickly describing, summarizing, analyzing circuit, based on some mathematical tricks, two of which we'll review today: Thevenin and Norton equivalent circuits.

- **Thevenin** — taking a complex circuit seen between two terminals and representing it as a resistor in series with a voltage source
 - **Norton** — taking a complex bit of circuitry between two terminals and representing it as a current source in parallel with a current source
1. These only apply to “linear circuits” that is, circuits made of (ideal) resistors, capacitors, inductors, op-amps, filters
 2. Non-linear elements include things like diodes, transistors, and some of the digital logic stuff we'll get into later in the semester.
 3. It might pay us dividends for us to consider what we mean by linearity at this point in the semester as it will become very relevant in our upcoming analyses

7.2 Linearity

Comprises two separate yet equally important properties

1. Homogeneity — If the input (the excitation) is multiplied by a constant, the output (the response) is multiplied by the same constant

$$v = iR \rightarrow kv = kiR$$

2. Additivity — The response to a sum of excitations is equal to the responses to each individual excitation

$$v_1 = i_1 R; v_2 = i_2 R; \rightarrow v = (i_1 + i_2)R = i_1 R + i_2 R = v_1 + v_2$$

Much of what we will do in this class is linear and much in life, given sufficient approximating, can be considered linear. Such relationships are useful, if not always strictly true (recall that even wires have resistivities and resistors have frequency ranges)

Note that since power is $i^2 R = v^2 / R$, the relationship is a quadratic and thus our necessary assumptions of linearity are not applicable.

7.3 Superposition

- Until now, weve been considering everything in a circuit always “on”, but one of the things the linearity of the system allows us to do is to selectively turn on and off sources while we solve, so long as we sum them up in the end.
- This principle — **superposition** — states that the voltage (or current) through an element (in a linear circuit) is the algebraic sum of the voltages across (or current through) that element due to each independent source acting alone.
- To apply the superposition principle
 1. Turn off all independent source but one and find the output (voltage or current) due to that source [using any of the techniques youve previously learned]
 2. Do this for each independent source
 3. Find the total contribution [for any given element, or indeed for all of them] by adding all the contributions due to the independent sources
 4. (Leave in all dependent sources since they are controlled by circuit variables)

- To turn off a source:

Voltage sources get replaced by a 0V source / a short circuit —
Turn voltage sources into wires

Current sources get replaced by a 0A source / an open circuit —
Cut current sources out

Example 4.5

For the circuit in Fig. 4.12, use the superposition theorem to find i .

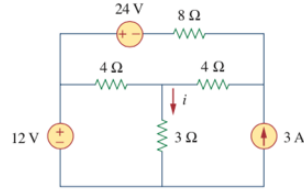


Figure 4.12
For Example 4.5.

Solution:

In this case, we have three sources. Let

$$i = i_1 + i_2 + i_3$$

where i_1 , i_2 , and i_3 are due to the 12-V, 24-V, and 3-A sources respectively. To get i_1 , consider the circuit in Fig. 4.13(a). Combining 4 Ω (on the right-hand side) in series with 8 Ω gives 12 Ω. The 12 Ω in parallel with 4 Ω gives $12 \times 4/16 = 3$ Ω. Thus,

$$i_1 = \frac{12}{6} = 2 \text{ A}$$

To get i_2 , consider the circuit in Fig. 4.13(b). Applying mesh analysis gives

$$16i_a - 4i_b + 24 = 0 \quad \Rightarrow \quad 4i_a - i_b = -6 \quad (4.5.1)$$

$$7i_b - 4i_a = 0 \quad \Rightarrow \quad i_a = \frac{7}{4}i_b \quad (4.5.2)$$

Substituting Eq. (4.5.2) into Eq. (4.5.1) gives

$$i_2 = i_b = -1$$

To get i_3 , consider the circuit in Fig. 4.13(c). Using nodal analysis gives

$$3 = \frac{v_2}{8} + \frac{v_2 - v_1}{4} \quad \Rightarrow \quad 24 = 3v_2 - 2v_1 \quad (4.5.3)$$

$$\frac{v_2 - v_1}{4} = \frac{v_1}{4} + \frac{v_1}{3} \quad \Rightarrow \quad v_2 = \frac{10}{3}v_1 \quad (4.5.4)$$

Substituting Eq. (4.5.4) into Eq. (4.5.3) leads to $v_1 = 3$ and

$$i_3 = \frac{v_1}{3} = 1 \text{ A}$$

Thus,

$$i = i_1 + i_2 + i_3 = 2 - 1 + 1 = 2 \text{ A}$$

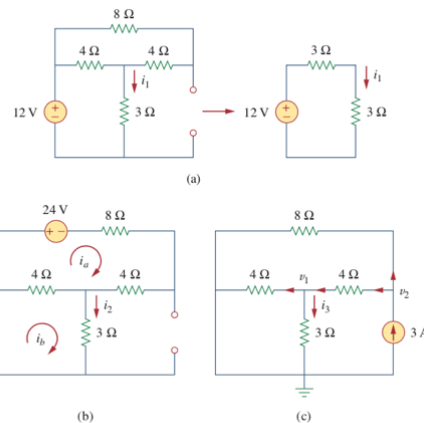


Figure 4.13
For Example 4.5.

7.4 Source transformation

Source transformation is the process of replacing a voltage source v_s in series with a resistor R by a current source i_s in parallel with a resistor R or

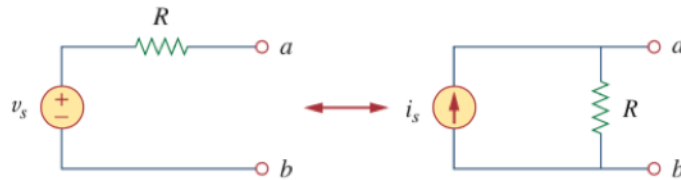


Figure 4.15

Transformation of independent sources.

vice versa.

- We can prove these two are equivalent between a-b by short circuiting the two-terminals.
- If the sources are turned off, the resistance at terminal a-b are the same (R)
- If the terminals are shorted, current flowing from a to b is $i_{ab} = V_s/R$ and $i_{ab} = i_s$. Thus $V_s/R = i_s$
- You can also replace dependent sources this way, provided you're careful, but we'll skip that analysis here and I won't encourage its use unless you personally feel comfortable with the material

7.5 Thevenin equivalents

- A linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source, V_{th} , in series with a resistor, R_{th}

V_{th} is equal to open-circuit voltage of original network, $V_{th} = V_{oc}$

- If we were to short the connection across terminals a and b, we can see (as we did previously), that $i_{sc} = V_{th}/R_{th}$

Thus the short-circuit current is equal to the current for the original circuit and the Thevenin equivalent.

- These two facts allow us to say something rather interesting, namely that the **Thevenin resistance** of a circuit is equal to the ratio of its open-circuit voltage and its short-circuit current. $R_{th} = V_{oc}/I_{sc}$

- Thus, to determine the **Thevenin equivalent circuit**, we start by analyzing the original network for its open-circuit voltage and its short circuit current. [A more robust derivation of this is shown in your book in chapter 4.7]

- To find the **thevenin equivalent resistance**:

*If there are **no** dependent sources*, turn off all independent sources in the network. R_{th} is the input resistance to the network between the two terminals of interest

*If **there are** dependent sources*, still turn off all independent sources and apply superposition.

Apply a voltage at the terminals and determine the resulting current. Then R_{th} is the ratio of applied voltage and elicited current v_o/i_o

Or apply a current and determine the resulting voltage. Use which ever you feel comfortable with.

7.5.1 An example

Create thevenin equivalent circuit between a and b [R_L is a potentiometer and thus its value can change. We want to simplify our understanding of how all the complex stuff before it will act.]

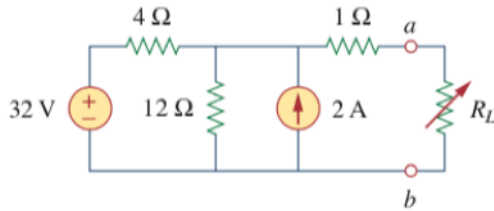


Figure 4.27

For Example 4.8.

1. Start by turning off the independent sources (32 V and 2 A), replacing them with a short- and an open-circuit respectively
2. This will yield our resistance as a $4 \text{ } \text{---} \text{ } 12 + 1 = (4*12)/16 + 1 = 4$ ohms
3. Next, identify what our V_{Th} would be
4. To find V_{Th} we can apply mesh analysis

$$32i_1 - 12i_1 + 12i_2 = 0 \quad (7.1)$$

$$i_2 = 2 \quad (7.2)$$

$$i_1 = 0.5A \quad (7.3)$$

$$(7.4)$$

then plug it in for the voltage across the 12 ohm

$$V_{th} = 12(i_1 - i_1) = 30 \quad (7.5)$$

5. Or could use nodal analysis

$$(32V_{th})/4 + 2 = V_{Th}/12 \rightarrow V_{Th} = 30 \quad (7.6)$$

7.6 Norton equivalents

- A linear two-terminal circuit can be replaced by an equivalent circuit comprising a current source, I_N in parallel with a resistor R_N

I_N is equal to the short-circuit current through the terminals

- To find the Norton equivalent resistance, we start the same way we did for R_{Th} — that is, short our voltage sources, open our current sources and find the resistance.

Well then this should suggest to us that R_N is equal to R_{Th} , and indeed they are equal.

- The Norton current, I_N , is equal to the short-circuit current.

So we merely find the current that would travel through the short

7.6.1 An example

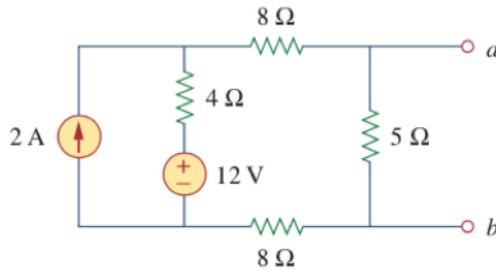


Figure 4.39

For Example 4.11.

1. We begin by zeroing all of our independent sources

$$R_N = 5 \parallel (8 + 4 + 8 \parallel 0) = 5 \parallel 20 = (5 * 20) / (5 + 20) = 4 \text{ ohms}$$

2. We can apply mesh analysis to find I_N

We can ignore the 5-ohm resistor as its in parallel with a short and current will always seek the path of least resistance.

Recall our bioimpedance example where with increasing frequency caused the current to flow down a different branch, because with greater frequency the capacitor went from acting like an open

circuit (at low frequencies) to a short circuit (at high frequencies), thus bypassing the other branch altogether.

$$I_1 = 2 \quad (7.7)$$

$$I_2 = 124i_2 + 4i_1 8i_2 8i_2 \rightarrow 4(2)20(i_2) = -12 \quad (7.8)$$

$$I_2 = 1 = i_{sc} = I_N \quad (7.9)$$

3. Alternatively, we could have found the Thevinin voltage [meshing it up]

$$i3 = 2 \quad (7.10)$$

$$12 - 4(i4) + 4(i1)8(i4) - 5(i4)8(i4) \rightarrow 4(2)25(i4) = -12 \quad (7.11)$$


$$I4 = 0.8A \quad (7.12)$$

Since we know 0.8 A goes through the 5 ohm resistor, and since we know that that 5 ohm resistor experiences the same voltage drop as the open circuit, we simple multiple $5 \cdot 0.8$ to give us, 4 V

4. Well since we know $R_N = R_{Th}$ is 4 and V_{Th} is 4: $I_N = V_{Th}/R_{Th} = 1A$
5. Thus Norton and Thevenin circuits are two sides of the same source transformation coin

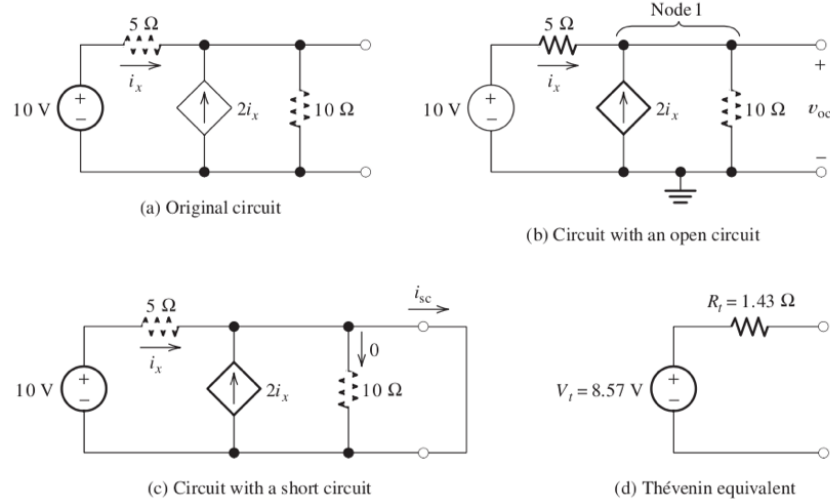7.7 Equivalentents with dependents

When weve got a dependent source, we cant just remove the sources and combine impedances. Instead, weve got to analyze the circuit to find the open-circuit voltage and the short-circuit current (and indeed such an approach will work in all cases, its just a little bit more work on our parts)



- Im personally a fan of finding the Thevenin open voltage because it just clicks with my brain a little better, but if you like the Norton short-circuit current, feel to take that approach
- So I apply nodal analysis

$$I_x + 2i_x V_{oc}/10 = 0 \rightarrow 3i_x = V_{oc}/10 \quad (7.13)$$

Next we write an expression for our controlling variable, i_x (7.14)

$$10V_{oc} = i_x(5) \rightarrow i_x = (10V_{oc})/5 \quad (7.15)$$

We can substitute this into our previous equation (7.16)

$$3 * (10 - V_{oc})/5 = V_{oc}/10 \rightarrow \mathbf{V_{oc} = V_{Th} = 8.57} \quad (7.17)$$

- Now we can consider the short-circuit conditions.

$$I_x + 2i_x i_{sc} = 0 \rightarrow 3i_x = i_{sc} \quad (7.18)$$

$$I_x = 10/5 = 2 \rightarrow \mathbf{I_{sc} = 3i_x = I_N = 6} \quad (7.19)$$

- From this, we can take the ratio of the open circuit voltage and the short circuit current and find the equivalent resistance of the network via Ohm's law: $8.57 \text{ V} / 6 \text{ A} = 1.43 \text{ ohms}$

7.8 A step-by-step procedure

1. Perform two of these:

Determine the open-circuit voltage $V_t = v_{oc}$

Determine the short-circuit current $I_n = i_{sc}$

Zero the independent sources and find the Thevenin resistance R_t looking back into the terminals. Do not zero dependent sources

2. Use the equations $V_t = R_t I_n$ to compute the remaining value
3. The Thevenin equivalent consists of a voltage source V_t in series with R_t
4. The Norton equivalent consists of a current source I_n in parallel with R_t

Chapter 8


A review of the material so far

02/07/2019

8.1 A set of exercises in preparation of the first Glorified Quiz

- Find the equivalent resistance of the following [“+” means “in series with”, “||” means “in parallel with”]:
 - $R_1 + R_2 || (R_3 + R_4)$
 - $(R_1 + R_2) || (R_3 + R_4)$
 - $R_1 + (R_2 + R_3 || (R_4 + R_5)) \text{---} R_6$
 - $(R_1 || R_2 || R_3) || (R_4 || R_5 || R_6) \text{---} (R_7 + R_8 || R_9)$
- To use superposition, one must turn off sources. A voltage source is replaced by what? A current source is replaced by what?
- A 5 F capacitor has accumulated a total charge of 1250 C. What is the voltage across the capacitor?
- Name each of the four types of dependent power sources and explain their functioning a bit beyond their name.
- The unit of current is the ampere, A. What are some equivalent units (for instance, what is its relationship to charge)?

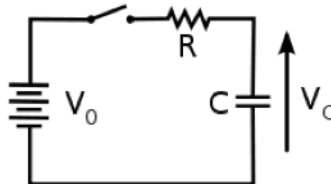6. Does potential change instantaneously over the terminals of a capacitor?
7. An RC circuit (in which “R + C”, seen below) has a time constant, $\tau = RC$. Prove the following at a time t_0 when the switch is thrown to complete the circuit.



- a. $I(t) = \frac{V_0}{R} \cdot e^{-t/\tau}$
 - b. $V(t) = V_0 (1 - e^{-t/\tau})$
 - c. $Q(t) = C \cdot V_0 (1 - e^{-t/\tau})$
8. What is the difference between active and passive circuit elements?
 9. What can an ideal current source do what a real one cannot?
 10. What can ideal voltage source do what a real one cannot?
 11. Draw the symbol for a polarized capacitor.
 12. Draw the symbol for a potentiometer.
 13. Draw an op-amp, label its terminals, and explain what each does.
 14. Whats another name for a conductor?
 15. Which way does current run in a diode?
 16. Describe what Ohms law tells us in your own words.
 17. What is conductance? State Ohms law using conductance. What does it tell us about eh current passing through conductive materials?
 18. What is the equation for resistance in terms of resistivity? If resistivity goes up, what happens to resistance? If the cross-sectional areas decreases, what results? If a resistor keeps the exact same cross-sectional area over a length L , yet we contorted it into a very weird shape (say a balloon-animal poodle), will its resistance remain the same according to the aforementioned equation. Does that agree with your intuition?

8.1. A SET OF EXERCISES IN PREPARATION OF THE FIRST GLORIFIED QUIZ77

19. A capacitor has a time variance of current according to the follow formulation $I(t) = \frac{dQ(t)}{dt} = C \frac{dV(t)}{dt}$. That might be useful to know. See if you can prove that relationship to yourself knowing that $C = Q/V$.
20. What is an inductor and how does it work?
21. What is impedance? What is impeded? What does the impeding?
22. What is the real and imaginary component of impedance.
23. How would I represent impedance by a magnitude and phase?
24. What is impedances inverse? What are its real and imaginary components?
25. What is the impedance of a resistor, capacitor, and inductor?
26. Find the equivalent impedance of the following, being sure to remove imaginary numbers from the denominator [“+” means “in series with”, “||” means “in parallel with”]:
 - a. $Z1 || (Z2 + Z3)$
 - b. $(R1 + C1) || C2 || (R2 + R3 + C3)$
 - c. $(R1 + L1) || (C1 + L1) || (C1 + R1)$
27. Convert a Wye circuit, with all $R = 10$ ohms, to a Delta circuit.
28. Find the equivalent impedance of a Delta circuit of capacitors.
29. Given the following map, can you plan a parade route that crosses each bridge exactly once? Why or why not?

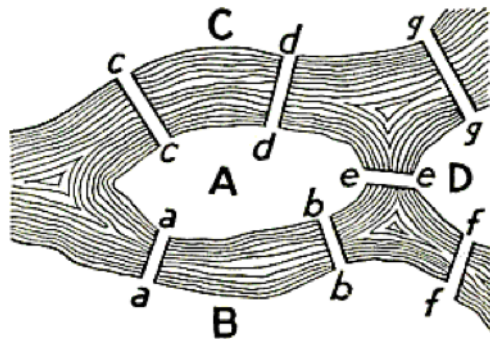


FIGURE 98. *Geographic Map:
The Königsberg Bridges.*

30. 32. Prove the fundamental theorem of network topology given any circuit (for instance, those aforementioned).
31. Kirchhoffs current law is a mere recitation of what other law of physics?
32. Kirchhoffs voltage law is a mere recitation of what other law of physics?
33. When do we most use KCL? When do we must use KVL? Which do you prefer in general and why?
34. Draw a complicated circuit (at least four branches) and solve for the current going through each component.
35. Analyze the aforementioned complicated circuit using nodal analysis. Analyze said circuit with mesh analysis. Prove the validity of the fundamental theorem of network topology using said circuit.
36. What is the difference between earth ground and chassis ground?
37. Draw a circuit using each of the following, $R1 = 10$ ohms, $R2 = 20$ ohms, $R3 = 30$ ohms, $R4 = 40$ ohms, $V1 = 20$ V, $V2 = 10$ V, and $I1 = 2$ A. Solve using nodal analysis if you can (do you need to make a supernode?). Solve using mesh analysis if you can (do you need to make a supermesh?).
38. Can you imagine modeling some actions in terms of circuits? For instance, if you were asked to model an equivalent circuit based on the operations of a shop floor, could you do it? If you were asked to model some aspect of physiology could you? The resistance of blood to flow? The capacitance of the lungs? The duration of our blinks?
39. What is Cramers rule and how do we use it?
40. Draw a circuit with at least five resistors and two current sources. Put that circuit into matrix formation for nodal voltages from inspection alone. What values should be along the diagonal, what values should be on the off-diagonal?
41. To solve the above circuit in MATLAB, what would you type in?
42. For any circuit stated previously, add a voltage source to one of the branches and solve using nodal analysis. What new technique did you need to employ and why did you need to? What does that technique do to our matrix?

8.1. A SET OF EXERCISES IN PREPARATION OF THE FIRST GLORIFIED QUIZ79

43. To any previously mentioned circuit, add a dependent current source and let it be dependent on the current going through R1. How does this change your nodal voltages?
44. Given a jolt of 240 J from an AED, provide an energy equivalent. For example, how many little soft kitten jumps on the chest (1 kg, 5cm) is it equivalent to? It would be like falling from a height of how much? [Hint: the ground comes up at you.]
45. A hospital consumes 500 kW in 60 seconds. How many people running on treadmills would it take to power it for a minute?
46. A nurse starts their shift turning on medical doohickey that consumes 50 W at 220 V. How many electrons worth of charge pass through the doohickey before the nurse turns it off at the end of their shift, 10 hours later?
47. Explain how mesh analysis works.
48. Draw a mesh circuit with at least 6 unique elements. Analyze it.
49. Draw another mesh circuit with at least four loops. Analyze it.
50. For the two above-mentioned mesh circuits, put them directly into matrix form. What values go along the diagonal? What values go on the off-diagonals?
51. For one of the mesh circuits you drew in either, add a dependent current source and solve using mesh analysis.
52. How do we measure current and potential using actual ammeters and voltmeters? Why must we break the circuit to measure current? How do we measure potential across an element?
53. Say, in as much detail as you can muster, what you believe the Thevenin circuit theorem is about.
54. Say, in as much detail as you can muster, what you believe the Norton circuit theorem is about.
55. Changing a potential source to a current source is an example of what technique to analyze circuits?
56. What are two attributes necessary for things to be “linear”?

57. What is superposition and how do we use it to analyze a circuit?
58. How do you turn off a voltage source in a circuit diagram? How do you turn off a current source?
59. To one of the above dozen or so circuits you have drawn, find the Thevenin equivalent.
60. To one of the above dozen or so circuits you have drawn, find the Norton equivalent.
61. To the Thevenin in 62, convert it to its Norton equivalent. To the Norton in 63, convert it to its Thevenin equivalent.
62. What is an open circuit? What is a short circuit? How are they relevant to Thevenin and Norton equivalents?
63. Draw an LM741 and label all 8 pins.
64. What is an operational amplifier? What does it behave like? What can it do for us? How are they different from resistors, capacitors, and their ilk?
65. What are the three key features we need to know to analyze op-amp circuits?
66. Draw an inverting amplifier with $R1 = 20$ ohms, and $R2 = 100$ ohms. What is the gain on the input signal?
67. Draw an inverting amplifier with $Z1 = R1 = (R_a || R_b)$ and $Z2 = R2 = (R_c + R_b)$. Solve for the output voltage in terms of the input voltage.
68. Draw a non-inverting amplifier with $R1 = 100$ kohms and $R2 = 100$ kohms.
69. Draw the two circuits you drew above in series with one another. What is the output?
70. What is a voltage follower and why is it important?
71. If its so important you should be able to draw one and analyze its operation! Lets do that. Draw a voltage follower and demonstrate its behavior in as much detail as you would need to convince another engineer you know what youre talking about.

8.1. A SET OF EXERCISES IN PREPARATION OF THE FIRST GLORIFIED QUIZ81

72. Why might we want to use a voltage follower with an electrocardiogram?
73. What is a summing amplifier?
74. A summing amplifier can actually act as a logic converter is set up right. Can you imagine using a set of summing amplifiers to determine a winner in a simple tic-tac-toe game in which button presses turned on new voltage sources? Briefly describe how you could determine a winner.
75. If I have a summing amplifier in which $V_1 = 10\text{ V}$, $R_1 = 10\text{ ohms}$, $V_2 = 10\text{ V}$, $R_2 = 10\text{ ohms}$, and $R_f = 20\text{ ohms}$, what is my output voltage?
76. What is a differential amplifier and why is it important?
77. Draw a differential amplifier. Analyze said differential amplifier. What is the output voltage in terms of the input voltage?
78. What is a transfer function?
79. You know how to go from a triangle (Delta) to a y (Wye) circuit for equivalence. How would you find the equivalent of going from a square to a cross?
80. Draw a blood vessel. Find the electrical equivalent across the vessel and through the vessel.
81. Draw the meanest circuit you think I'd ever give you on an exam. Then add a voltage dependent voltage source to one branch of it (its dependence rests on you). Solve it using nodal analysis, mesh analysis, superposition, and just plain looking at it.

A Glorified Quiz I

Given on February 12, 2019. All problems worth 10 points. Do not spend an inordinate amount of time on any given problem. Try your best.

Contents

8.1	A set of exercises in preparation of the first Glorified Quiz	71
8.2	Problem 1 on basic impedance	80
8.3	Problem 2 on basic knowledge	80
8.4	Problem 3 on current and potential	80
8.5	Problem 4 on transresistance amplification or bioamplification	81
8.6	Problem 5 on equivalent impedance	81
8.7	Problem 6 on differential amplification	81
8.8	Problem 7 on counting cells	81
8.9	Problem 8 on your own	82
8.10	Problem 9 also on your own	82
8.11	Problem 10 on miscellanea	82
8.12	Useful equations in alphabetical order	83

8.2 Problem 1 on basic impedance

Find the equivalent impedance of the following (“+” means “in series with” and “||” means “in parallel with”) being sure that you end up with no imaginary terms in denominators. It may be helpful to draw these circuits as you understand them.

- 1.
- 2.
- 3.

8.3 Problem 2 on basic knowledge

- 1.
- 2.
- 3.
- 4.
- 5.

8.4 Problem 3 on current and potential

A current, $i(t)$, enters a device, causing a potential drop, $v(t)$. The current and the potential can be described mathematically as

$$i(t) = \begin{cases} 0 \text{ A}, & t < 0 \\ f(t) \text{ mA}, & t \geq 0 \end{cases}$$

$$v(t) = \begin{cases} 0 \text{ V}, & t < 0 \\ g(t) \text{ V}, & t \geq 0 \end{cases}$$

- 1.
- 2.
- 3.

8.5 Problem 4 on transresistance amplification or bioamplification

There are at least two kinds of current-to-voltage converters (also known as *transresistance amplifiers*).

8.6 Problem 5 on equivalent impedance

Choose one of the following (or do both for bonus points).

1. Determine the equivalent impedance seen between terminals a and b.
2. Determine the equivalent impedance of a three-dimensional network of resistors, each of value R , as measured from the two farthest corners.

8.7 Problem 6 on differential amplification

1. What is the potential difference between points a and b?
2. What is the gain seen between points a and b?
3. What is the current running through R_2 ?
4. What is the current running through R_4 ?
5. If the operational amplifier (LM741) were only supplied 10 V, what is the largest V_1 we could input before our output was saturated?

8.8 Problem 7 on counting cells

A Coulter counter (an electronic means by which to count the number of cells passing by a channel) is essentially a bridge circuit that determines the presence of a cell by tracking a change in due to a change in resistance from the cell. Referring to the circuit below, $R_1 = R_2 = R_3 = R_4 = R$ at rest (no cells present) and every time a cell passes through the channel R_2 increases its resistance by ΔR .

- 1.
- 2.
- 3.

8.9 Problem 8 on your own

1. Set up the series of simultaneous equations to **find the mesh currents**.
2. Determine **the matrix form** of the simultaneous equations.
3. Determine **the power dissipated** by three of your resistors.
4. Find **the equivalent resistance** of the system as measured from the two most distant corners of your circuit drawing.

8.10 Problem 9 also on your own

1. Determine whether your circuit **satisfies the fundamental theorem of network topology**.
2. **Determine the nodal voltages** (*at the very least set them up as a solvable set of simultaneous equations and try to solve them*).
3. **Determine the current** going through three of your resistors.

8.11 Problem 10 on miscellanea

- 1.
- 2.
- 3.

8.12 Useful equations in alphabetical order

$$\begin{aligned}
 b &= l + n - 1 \\
 C &= \frac{Q}{V} \rightarrow i(t) \frac{dQ(t)}{dt} = C \frac{dV(t)}{dt} \\
 \text{Cramer's Rule: } x &= \frac{D_1}{D}, y = \frac{D_1}{D} \text{ for } a_1x + b_1y = c_1, a_2x + b_2y = c_2 \\
 \text{where } D &= \begin{bmatrix} a_1 & b_1 \\ a_2 & b_2 \end{bmatrix}, D_1 = \begin{bmatrix} c_1 & b_1 \\ c_2 & b_2 \end{bmatrix}, D_2 = \begin{bmatrix} a_1 & c_1 \\ a_2 & c_2 \end{bmatrix} \\
 \mathbf{E} &= \rho \mathbf{J} \\
 E &= pt \\
 e &= -1.602 \cdot 10^{-19} \text{ C} \\
 i &= \frac{dq}{dt} \\
 i_N &= i_{sc} = V_{Th}/R_{Th} \\
 \text{KCL: } \sum_{x=1}^n i_x &= 0 \\
 \text{KVL: } \sum_{x=1}^n v_x &= 0 \\
 L &= \frac{\Phi}{I} \rightarrow v(t) = \frac{d\Phi}{dt} \\
 p &= \frac{dw}{dt} \\
 Q &= \int_{t_1}^{t_2} i(t) dt \\
 R &= \rho \frac{l}{A} \\
 v &= \frac{dw}{dq} \\
 v &= iR \\
 V_{Th} &= V_{oc} \\
 \mathbf{Z} &= R + jX = |\mathbf{Z}|e^{j\theta} \\
 \text{Parallel: } \frac{1}{Z_{eq}} &= \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots \\
 \text{Series: } Z_{eq} &= Z_1 + Z_2 + Z_3 + \dots
 \end{aligned}$$

Part II

Systems

Chapter 9

The Laplace Transform: I. What it is and why it is important

02/14/2019 Lecture 9.

Contents


9.1	Euler's formula, Euler's identity	88
9.2	The Laplace transform	89
9.3	The Laplace transform of 1	90
9.4	The s -plane	91
9.5	The linearity of the Laplace transform	93
9.6	The Laplace transform of e^{at}	93
9.7	The Laplace transform of dx/dt	94
9.8	The Laplace transform of \sin	96
9.9	The Laplace transform of $\int_0^t x(u)du$	96
9.10	The Laplace transform in RLC circuits	97
9.10.1	Resistors	97
9.10.2	Inductors	97
9.10.3	Capacitors	98
9.10.4	RLC circuits	99

9.1 Euler's formula, Euler's identity

You must all know, from this moment on, that Euler's formula is thus

$$e^{jx} = \cos x + j \sin x \quad (9.1)$$

where e is Euler's number, j is the imaginary unit, and \cos and \sin are trigonometric functions cosine and sine respectively. This is a very unique relationship in the history of mathematics because it combines so much of our tools in mathematics. It has an exponential, it has a variable, it's got all of trigonometry, and it's even got this orthogonal reality of the "imaginary" domain. The formula describes how a vector on the complex manifests as a function of the variable x alone. The implications of this will be appreciated with a time and effort on our parts.

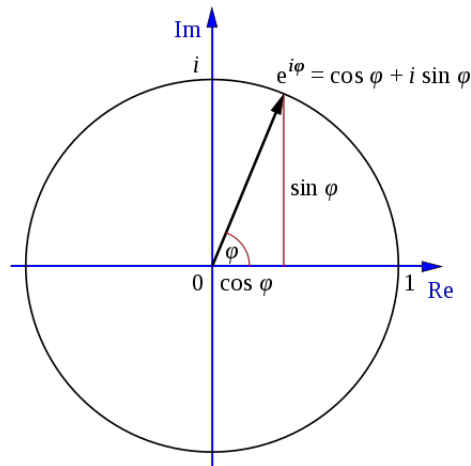

There is a special case of this formula known as Euler's identity and regardless of the number of times I prove it to myself, I just can't believe it all works out like this. If $x = \pi$ then

$$e^{j\pi} = -1 \quad (9.2)$$

which has just about every important mathematical thing in it: exponentials, imaginary numbers, constants of the universe, negative numbers, the single unit. In fact, add the one back to the other side and you'll see a zero appear from the depths. All this to say, recognizing the interrelatedness of exponential functions to just about everything else in mathematics and engineering will help us here and elsewhere immensely.

9.2 The Laplace transform

Mathematically, the Laplace transform is simple to describe. First, get yourself a curly L, looks like this

$$\mathcal{L} \tag{9.3}$$

Next to that \mathcal{L} , put some curly brackets, like so

$$\mathcal{L}\{\} \tag{9.4}$$

Within those brackets put some function, say one of time, $f(t)$

$$\mathcal{L}\{f(t)\} = \text{The Laplace transform of } f(t) \tag{9.5}$$

We may also, sometimes, take a function's name, say $f(t)$, capitalize it, $F(t)$, and call that the Laplace transform. I am not personally the biggest fan of this notation as it can become quite distracting and confounding when combined with other transforms you might want to one day use, such as Fourier transforms, Hilbert transforms, and so on.

I prefer to designate my Laplace transforms with a squiggly sign over a capitalized version of the function name, like so

$$\mathcal{L}\{f(t)\} = \tilde{F}(s) \tag{9.6}$$

That squiggly line, and many of those that follow, help explain what the Laplace transform is kind of doing to the reality around you. It's seeing relationships outside of time, cast in a plane of infinite exponential sine waves, with bottomless zeros and infinities you can draw a small circle around. The Laplace transform, should be, I believe, a transformative way of viewing the world around you. The power of the Laplace transform (and its ilk) is to reveal useful realities to us and our machines. Turns out there's more to life than just the time ahead of us. And we can usefully describe it.

Some of those astute among you will notice I tried to slip something by you in the above definition. (Those of you glancing over the mathematics, get yourself back in the habit of *reading* mathematics, out loud if need be. Make sure you understand what I'm saying before agreeing to it.) What I tried to sneak into this definition is a new variable s that somehow our function, $f(t)$, became in terms of when transformed. We will get into the more mystical nature of the s -plane and its variable s , but for now, let's just call it some dummy variable. To you, at this point, it is just some stranger

you've met in the street. You don't know them at all. First thing you've got to do, is say, Hello.

Before any of that, though, we must get to the definition of the definition of the Laplace transform. It is what we do to a function $f(t)$ to yield another equation $\tilde{F}(s)$. In that sense, the Laplace transform is defined as

$$\mathcal{L}\{f(t)\} = \int_0^{\infty} e^{-st} f(t) dt \quad (9.7)$$

which is to say it is the integral over all of time of the product of our function $f(t)$ with an exponential function raised to a power of time, t , scaled negatively with some dummy variable, s . Essentially, if I were to multiple my function, $f(t)$ at every point in time with a probing function e^{-st} and summed it all up, what would I get? And more importantly to all of this, what would it tell me?

Another way of thinking about what the Laplace transform is “doing” is to think about what the mathematics itself is proposing to do. It's taking some function, $f(t)$, and wrapping it along a real and an imaginary exponential, producing both sines and cosines.

9.3 The Laplace transform of 1

Let me start off with the simplest number I can think of, sophist that I am. What is the Laplace transform of the number 1. If I can't solve this integral for the number 1, what the heck can I do? So let's convince ourselves that we can solve at least that much.

$$\mathcal{L}\{f(t)\} = \mathcal{L}\{(1)\} = \int_0^{\infty} e^{-st}(1)dt \quad (9.8)$$

Some, at this point, might be concerned with that ∞ up there in this integral. It creates what is sometimes called an improper integral, that is, one which has either (or both) limits of infinity or an integrand that approaches infinity at one or more points in the range of integration¹. To get around this improperness, we create for ourselves yet another dummy variable, let's call this one A . Thus we can also write the Laplace transform as

$$\mathcal{L}\{(1)\} = \int_0^{\infty} e^{-st}(1)dt = \lim_{A \rightarrow \infty} \int_0^A e^{-st}(1)dt \quad (9.9)$$

¹This latter fact forms much of the basis of our understanding of control theory.

which is the integral from 0 to A – which we can do – evaluated, ultimately, as A goes infinitely. We take the antiderivative, bounded by our limits, to be

$$\lim_{A \rightarrow \infty} \int_0^A e^{-st}(1)dt = \lim_{A \rightarrow \infty} \left[-\frac{1}{s}e^{-st} \right]_0^A \quad (9.10)$$

$$= \lim_{A \rightarrow \infty} \left[\left(-\frac{1}{s}e^{-sA} \right) - \left(-\frac{1}{s} \right) \right] \quad (9.11)$$

$$= \lim_{A \rightarrow \infty} \left[-\frac{1}{s}e^{-sA} + \frac{1}{s} \right] \quad (9.12)$$

Let us think about what our limit does. In this case the only factor with an A involved is $-\frac{1}{s}e^{-sA}$. Here, if A becomes huge, it knocks against that s , getting even bigger, and knocks against that negative sign to become very very negative. Having a very very negative negative number in our exponential function causes it to go screaming down to 0. In this case, the case where the function $f(t) = 1$, upper infinite limit has obliterated the term associated with it, whereas the lower limit has preserved the term associated with it. This leaves us with the final result:

$$\mathcal{L}\{f(t)\} = \frac{1}{s} \quad (9.13)$$

9.4 The s -plane

Where some see time, others see cycles, decay. The s -plane allows us to describe the physical world around us and much of the activity that occurs therein as a bunch of sines and exponentials, which is a quite clever way of squinting at a world that's always got us looking across time. Instead of charting a function or describing some behavior (perhaps of some system) as an amplitude changing over time, let us consider what such a function might look like if on one axis we had a variable describing how fast it decays over time and on the other axis we described how hard the system rattles at each frequency. In plotting such a function, one could see how a system will react under a myriad of conditions which you literally do not have the time to do if you confine yourself to just this slice of reality.

And so we must turn orthogonally to the only world we've ever known and stare into the s -domain.

We can start by taking a peak at our variable, s . For our first use of the Laplace transform, we didn't even need to know what s was to work with it and to get an answer (of some sort). Indeed I took to calling it a

dummy variable since the mechanical evaluation of the mathematics does not require it. It is important to make sure you can always do the math if you are ever called upon to do so. For much of what follows clear and clever shorthand will help us to view signals in a multitude of ways, including our bundling up of terms within s . As with much in life and in this class, s comprises a real component, σ and an imaginary component, ω :

$$s = \sigma + j\omega \quad (9.14)$$

By themselves these two parameters are underwhelming. When raised as the exponent to an exponential and they start to describe a whole other world. Whether it has been stressed to you in your differential equations class or not, every single differential equation in the world has as at least one of its solutions the combination of exponential functions with and sine (or cosine) waves. The reasons for this range from the philosophic (we are trapped between repetition and degradation) to the mechanical (the derivatives of exponentials and sines and just scaled exponentials and sines). Let us take a look at the form s takes itself for the Laplace transform:

$$e^{-st} = e^{-(\sigma+j\omega)t} \quad (9.15)$$

If we were to expand it out, we could perhaps convince ourselves that two separate yet equally important components emerge. One describes a function which dampens a response with time and one which oscillates back and forth with time.

$$e^{-(\sigma+j\omega)t} = \underbrace{e^{-\sigma t}}_{\text{damping}} + \underbrace{e^{-j\omega t}}_{\text{sinusoids}} \quad (9.16)$$

The first of these behaviors we can probably prove to ourselves by inspection. If $s > 0$, and let us say that it is, then as t gets really large, the exponential function will die down to zero, under the influence of that negative infinity. Therefore, we are right to call $e^{-\sigma t}$ a damping term, since it will eventually smooth everything away to nothingness.

The second of these behaviors requires a brief detour back to our Eulerian days².

A benefit to this whole situation is that it reduces the mathematical complexity of the reality of the situation (represented by the mathematical operation of convolution, which we will get to in a couple weeks) to algebra.

²One should get use to thinking in both Eulerian and Laplacian terms.

9.5 The linearity of the Laplace transform

The Laplace transform has at least one property that we must address here, its linearity. As the transform satisfies the two conditions of linearity previously established, homogeneity (a response is proportional to an excitation) and additivity (a response is the sum of excitations), we can use it with near reckless abandon for linear systems, i.e., those we will concern ourselves with here.

The linearity of the transform means that the transform of a sum is that same as the sum of individual transforms. Moreover, scaling constants are not affected by the transform and remain constant throughout. Mathematically this may all be stated as:

$$\mathcal{L}\{a_1 f_1(t) + a_2 f_2(t)\} = a_1 \tilde{F}_1(s) + a_2 \tilde{F}_2(s) \quad (9.17)$$

This result is convenient for more involved analyses and is one we must keep in mind.

9.6 The Laplace transform of e^{at}

To apply the Laplace transform, we take our $f(t)$, multiple it by our probing function, e^{-st} , and integrate over all time (for the moment, let us stipulate $s > a$):

$$\tilde{F}(s) = \mathcal{L}\{f(t)\} = \int_0^\infty e^{-st} e^{at} dt \quad (9.18)$$

$$= \int_0^\infty e^{(a-s)t} dt \quad (9.19)$$

$$= \int_0^\infty e^{-(s-a)t} dt \quad (9.20)$$

$$= \left[-\frac{e^{-(s-a)t}}{s-a} \right]_0^\infty \quad (9.21)$$

$$= \left(-\frac{e^{-(s-a)\infty}}{s-a} \right) - \left(-\frac{e^0}{s-a} \right) \quad (9.22)$$

$$= 0 + \frac{1}{s-a} \quad (9.23)$$

$$\mathcal{L}\{e^{at}\} = \frac{1}{s-a} \quad (9.24)$$

From this we can perhaps see a pattern or two. Our Laplace transform took the exponent of the exponential and dropped it down in the denominator with s as a subtractive component. Thus, one might just as well commit to memory that that Laplace transform of e^{4t} is $\frac{1}{s-4}$ as look it up in a table. From this simple derivation we now know that $e^{-0.25t}$ transforms to $\frac{1}{4s+1}$ and could even convince ourselves that $3e^{-2t}$ becomes $\frac{3}{s+2}$. In fact, hopefully we can recognize that our previous derivation of the Laplace transform of the number 1 is just the case where $a = 0$ when $f(t) = e^{at}$.

You might wonder, what do I care about having a new fraction? What good does that do me? Already it has told you something you likely didn't know: as the values of a and s approach equality, the fraction blows up to infinity. We have what we call a "pole" at $s = a$.

9.7 The Laplace transform of dx/dt

Generally one does not spend a lot of time working through the mathematical conjuring of taking the Laplace of a derivative. The reason for this is because its final form is easy to learn, memorize, and deploy readily.

Let us begin with a simple, perhaps much too simple, example.

$$\frac{dx}{dt} - ax = 0 \quad (9.25)$$

Leveraging what we've learned of the linearity of our technique, let's find the Laplace transforms each portion of that equation.

$$\text{Laplace transform 1} = \int_0^\infty e^{-st} \frac{dx}{dt} dt \quad (9.26)$$

$$\text{Laplace transform 2} = \int_0^\infty e^{-st} x dt \quad (9.27)$$

The latter equation, "Laplace transform 2" is just another way of saying $\mathcal{L}\{x(t)\}$, so we can feel comfortable simply labeling that as $\tilde{X}(s)$.

The former equation requires us to integrate by parts. I will be assumed here that some calculus teacher somewhere once taught you the importance of integration by parts. It will be further assumed here that you know how to do it or could figure out how to do it if called upon to do so. As such, I will not belabor its implementation here and instead present my formulation

of the logic of the situation for you to follow:

$$\mathcal{L} \left\{ \frac{dx}{dt} \right\} = \int_0^\infty e^{-st} \frac{dx}{dt} dt \quad (9.28)$$

$$= - \int_0^\infty x(t) (-se^{-st} dt) + [xe^{-st}]_0^\infty \quad (9.29)$$

$$= s \int_0^\infty x(t) (e^{-st} dt) + [(xe^{-\infty}) - (xe^0)] \quad (9.30)$$

$$= s\tilde{X}(s) - x(0) \quad (9.31)$$

What this end result suggests to us, is that the Laplace of the derivative of some function $x(t)$ is the Laplace of the function itself, $\tilde{X}(s)$, multiplied by s to which an initial condition, $x(0)$ is subtracted.³

Combining these two results and rewriting:

$$\mathcal{L} \left\{ \frac{dx}{dt} - ax = 0 \right\} \rightarrow \mathcal{L} \left\{ \frac{dx}{dt} \right\} - \mathcal{L} \{ax\} = \mathcal{L} \{0\} \quad (9.37)$$

$$s\tilde{X}(s) - x(0) - a\tilde{X}(s) = 0 \quad (9.38)$$

$$\tilde{X}(s)(s - a) = x(0) \quad (9.39)$$

$$\tilde{X}(s) = \frac{x(0)}{s - a} \quad (9.40)$$

Without too much squinting, we can probably see that such a form is quite close to what we found for our exponential function's transformation, $\frac{1}{s-a}$. In fact, as will become clearer and more comfortable to you over time, is that indeed we can begin to quickly map a solution to a differential equation by first transforming it over the s -domain. In this particular case, we can

³In fact, we can expand this to n -th order derivatives. It will be of the form:

$$\mathcal{L} \left\{ \frac{dx}{dt} \right\} = s\tilde{X} - x(0) \quad (9.32)$$

$$\mathcal{L} \left\{ \frac{d^2x}{dt^2} \right\} = s^2\tilde{X} - sx(0) - \frac{dx(0)}{dt} \quad (9.33)$$

$$\mathcal{L} \left\{ \frac{d^2x}{dt^2} \right\} = s^2\tilde{X} - sx(0) - x'(0) \quad (9.34)$$

$$\mathcal{L} \left\{ \frac{d^3x}{dt^3} \right\} = s^3\tilde{X} - s^2x(0) - sx'(0) - x''(0) \quad (9.35)$$

$$\mathcal{L} \left\{ \frac{d^4x}{dt^4} \right\} = s^4\tilde{X} - s^3x(0) - s^2x'(0) - sx''(0) - x'''(0) \quad (9.36)$$

hazard a guess that a solution to the differential equation $\frac{dx}{dt} - ax = 0$ is the function $x(t) = x(0)e^{at}$, which indeed from inspection appears to work.

If you didn't catch it there, let me point it out here: you have just learned a very neat mathematical trick for an engineer. This might be the quickest way to solve a differential equation that you will ever know of.

We've taken a differential equation and reduced it to simple algebra.

9.8 The Laplace transform of \sin

There are many ways of going about proving this to yourself. This is the one I prefer. It forces us to begin, as we should, with Euler's formula.

$$\mathcal{L}\{\sin at\} = \mathcal{L}\left\{\frac{e^{iat} - e^{-iat}}{2i}\right\} \quad (9.41)$$

$$= \frac{1}{2i} (\mathcal{L}\{e^{iat}\} - \mathcal{L}\{e^{-iat}\}) \quad (9.42)$$

$$= \frac{1}{2i} \left(\frac{1}{s - ia} - \frac{1}{s + ia} \right) \quad (9.43)$$

$$= \frac{1}{2i} \left(\frac{s + ia - s + ia}{s^2 + a^2} \right) \quad (9.44)$$

$$= \frac{1}{2i} \left(\frac{2ia}{s^2 + a^2} \right) \quad (9.45)$$

$$= \frac{a}{s^2 + a^2} \quad (9.46)$$

9.9 The Laplace transform of $\int_0^t x(u)du$

We have shown that taking the derivative of a function in the time domain is analogous to multiplying its Laplace transform by s in the frequency domain. Using integration by parts, we can similarly show that taking the integral of a function is analogous to dividing its Laplace transform by s . (Source: <https://www.youtube.com/watch?v=IYOzTt-gB8A>)

9.10 The Laplace transform in RLC circuits

9.10.1 Resistors

To find the voltage drop across a resistor we apply Ohm's law, $v = iR$. To go from the time-domain to the Laplace-domain for is notationally simple:

$$v(t) \rightarrow \tilde{V}(s) \quad (9.47)$$

$$i(t) \rightarrow \tilde{I}(s) \quad (9.48)$$

$$v(t) = i(t)R \rightarrow \tilde{V}(s) = \tilde{I}(s)R \quad (9.49)$$

That is, the voltage drop in the s -domain is equal to the current in the s -domain, scaled to the resistance, R .

9.10.2 Inductors

$$v(t) \rightarrow \tilde{V}(s) \quad (9.50)$$

$$i(t) \rightarrow \tilde{I}(s) \quad (9.51)$$

$$v(t) = L \frac{di(t)}{dt} \quad (9.52)$$

Recall from a previous section that the Laplace of a derivative, $\mathcal{L}\{\frac{dx}{dt}\}$ is equal to the product of the Laplace of the original function and s (with the initial conditions subtracted): $s\tilde{X}(s) - x(0)$. We can apply this same logic to solve the above problem, yielding the inductor's behavior:

$$v(t) = L \frac{di(t)}{dt} \quad (9.53)$$

$$\tilde{V}(s) = L(s\tilde{I}(s) - i(0)) \quad (9.54)$$

$$\tilde{V}(s) = sL\tilde{I}(s) - Li(0) \quad (9.55)$$

We can even redraw the circuit to see it as we would from the s -domain. If I've got a circuit, that starts with a horizontal wire with a current $\tilde{I}(s)$ going through it, I've currently got a potential of $\tilde{V}(s)$ at the rightmost end of that wire. Connecting that wire vertically, we can walk across our equation and see what it's telling us. Our first element is going to affect the current by $sL\tilde{I}(s)$. That's our inductor. We continue our KVL-inspired walk and see that we have a negative drop (a rise) in potential equal to $Li(0)$, the current at our initial condition scaled to our inductor's size. This is a potential source. From this, we have a new vantage point to survey

circuits from. Where before we thought of voltage sources as blackboxes, there's a curious response that gets induced in them.

If we were to solve for $\tilde{I}(s)$ by rearranging the equation

$$\tilde{I}(s) = \frac{\tilde{V}(s)}{sL} + \frac{i(0)}{s} \quad (9.56)$$

and we can redraw this as a parallel circuit. Or essentially, we are losing $\tilde{I}(s)$ through a node with two branches (see the two components on the right hand side). So for our rightmost branch we have a current source, scaled to $1/s$, and then we have our inductor, with an inductance of sL .

This technique is extensible to other electronic components. And is in fact another way of transforming our circuits, should the need or desire arise, more specifically source transformation with voltage sources in series with an inductor and current source in parallel with an inductor.

9.10.3 Capacitors

Imagine you've got current going into a capacitor and it's forming a potential on either side of it. we can describe this as

$$i = C \frac{dv}{dt} \quad (9.57)$$

We can take the Laplace of both sides

$$\mathcal{L}\{i\} = \mathcal{L}\{C \frac{dv}{dt}\} \quad (9.58)$$

$$\tilde{I}(s) = C(s\tilde{V}(s) - v(0)) \quad (9.59)$$

$$\tilde{I}(s) = Cs\tilde{V}(s) - Cv(0) \quad (9.60)$$

which is to say we have a current, $\tilde{I}(s)$, being divvied up at a node between two branches. The rightmost branch is a source, $v(0)$, scaled by a capacitance, C . (And because it's negative, it turns out this branch is actually entering the node just like $\tilde{I}(s)$). The other branch is a capacitor, $1/C$, multiplied by s .

Just as before with the inductor we can also imagine transforming this source. The simplest way I can think to prove that to ourselves is to rearrange our equation

$$\tilde{V}(s) = \frac{1}{sC} \tilde{I}(s) + \frac{v(0)}{s} \quad (9.61)$$

From this we can see that our potential drop across a series connected components, $\tilde{V}(s)$ is first dropped by a capacitor $1/sC$, and then dropped by a source, $v(0)$ scaled to s .

$$v(t) = \frac{1}{C} \int_{t_1}^{t_2} \quad (9.62)$$

9.10.4 RLC circuits

Combining these results and recognizing the linearity of each, in a series RLC circuit, we can merely add these all up to yield:

$$Ri(t) + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^{\tau=t} i(\tau) d\tau = v(t) \quad (9.63)$$

An example

What is the Laplace transform of a series RLC circuit with $L = 1$, $R = 7$, and $C = 10$.

Chapter 10

The Laplace Transform: II. How to use it

02/19/2019

Contents

10.1 A brief review	102
10.2 Two important places, zeros and poles	103
10.3 The general form of just about all systems . . .	104
10.3.1 Undamped systems	104
10.3.2 Underdamped systems	105
10.3.3 Critically damped systems	105
10.3.4 Overdamped systems	105
10.4 “Inverting” the Laplace transform	106
10.4.1 A convenient way of doing it	106
10.5 Worksheet	107
10.5.1 Problem 1	107
10.5.2 Problem 2	107
10.5.3 Problem 3	107
10.5.4 Problem 4	108
10.5.5 Problem 5	108

10.1 A brief review

Returning for a moment to our series RLC circuit from last time, once converted with the Laplace transform, the system is described via a second-order polynomial.

$$v_L = L \frac{di_L(t)}{dt} \quad (10.1)$$

$$v_R = i_R(t)R \quad (10.2)$$

$$v_C = \frac{1}{C} \int_0^t i(\tau) d\tau + V_c(0) \quad (10.3)$$

When all elements are placed in series, a simple KVL walk will suggest to us that

$$L \frac{di_L(t)}{dt} + i_R(t)R + \frac{1}{C} \int_0^t i(\tau) d\tau + V_c(0) = 0 \quad (10.4)$$

Transforming via Laplace¹:

$$L(s\tilde{I} - I_0) + R\tilde{I} + \frac{\tilde{I}}{sC} + \frac{V_0}{s} = 0 \quad (10.5)$$

$$s^2\tilde{I} - sI_0 + s\frac{R}{L}\tilde{I} + \frac{\tilde{I}}{C} + V_0 = 0 \quad (10.6)$$

Rearranging and rewriting

$$\tilde{I} = \frac{sI_0 - \frac{V_0}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \quad (10.7)$$

If we give to our RLC circuit the values of $L = 1$, $R = 7$, and $C = 10$ and initial conditions $V_0 = 10$ and $I_0 = 1$ we can see, without too much effort that the equation becomes

$$\tilde{I} = \frac{s - \frac{10}{1}}{s^2 + \frac{7}{1}s + \frac{1}{1 \cdot 10}} \quad (10.8)$$

$$\tilde{I} = \frac{s - 10}{(s + 2)(s + 5)} \quad (10.9)$$

In this form, we now see laid bare before us two important places in the s -domain: poles and zeros.

¹It may do you some good to remember that in the Laplace domain, differentiation is achieved by multiplying by s and integration is accomplished by dividing by s .

10.2 Two important places, zeros and poles

It may help us to recall that a point in the s -domain characterizes a system's response as a combination of decay, growth, and oscillations. Thus, since s is a coefficient of an exponential function, any value thereof will tell us whether the function

- will grow with respect to time ($\sigma > 0$);
- will decay with respect to time ($\sigma < 0$);
- will oscillate over time (s has an imaginary component); or
- will remain constant ($\sigma = 0$).

A system can be characterized by its combination of these behaviors by finding the roots of s for the system as described in the s -domain. These can either be a “zero” or a “pole”.

In our systems, as the value of s approaches

- a **zero**, the numerator of the transfer function approaches 0 and thus so too does the whole system and
- when approaching a **pole**, the denominator of the transfer function approaches 0, causing the system to approach the infinite.

Recalling our RLC circuit:

$$\tilde{I} = \frac{s - 10}{(s + 2)(s + 5)} \quad (10.10)$$

For this system, we have three special points.

1. $s \rightarrow 10$ causes the numerator to approach 0 (**and is thus a zero**) and so too will the system;
2. $s \rightarrow -2$ causes the denominator to approach 0 (**and is thus a pole**), causing the system response to be quite large; and
3. $s \rightarrow -5$ also causes the denominator to approach 0 (**and is thus a pole**), causing the system response to be quite large.

10.3 The general form of just about all systems

As it turns out, most systems on earth and else can be expressed by a generalized second-order equation

$$s^2 + 2\zeta\omega_n s + \omega_n^2 = f(t) \quad (10.11)$$

where ζ is the damping coefficient and ω_n is the natural frequency of the system, and $f(t)$ is some “forcing” function.

In our case, $\zeta = \frac{R}{2}\sqrt{\frac{C}{L}}$ and $\omega_n = \sqrt{\frac{1}{LC}}$

- **The natural frequency** is the frequency at which a system tends to oscillate in the absence of any driving or damping forces. It’s just what wants to happen.
- **The damping coefficient**, or the damping ratio, is a dimensionless measure of decay. It describes how oscillations in a system die down after a disturbance.

For the moment, we will consider systems for which $s < 0$. These systems are guaranteed to be “stable” in the sense that they will not grow exponentially large. Rather, given the fullness of time, we are assured that each of these types of systems will eventually decay away to a stable point.

10.3.1 Undamped systems

When $\zeta = 0$, a system comprises a single harmonic oscillator, as is the case of a mass suspended by a perfect spring. This is what we would expect with no “real” components ($e^{j\omega_n t}$)

- Two imaginary poles at $\pm j\omega_n$
- Undamped sinusoid with frequency equal to the imaginary part of the pole.
- Solution: $f(t) = A \cos(\omega_n t - \phi)$

²It may be more intuitive to think of this terms instead as $\zeta = \alpha/\omega_n$, where $\alpha = R/2L$ represents an attenuation coefficient (of units nepers/second).

10.3.2 Underdamped systems

When $0 < \zeta < 1$, a system will initially oscillate in response to a disturbance before dying down to zero. Can be described by the function $e^{j\omega_n \sqrt{1-\zeta^2}t}$

- Two complex poles at $-\sigma \pm j\omega_d$
- Damped sinusoid with exponential envelope. Time constant is equal to the reciprocal of the pole's real part.
- Solution: $f(t) = Ae^{-\sigma t} \cos(\omega t - \phi)$

10.3.3 Critically damped systems

When $\zeta = 1$, a system decays away as fast as possible with no oscillations or “overshoots”. As you might expect, this is a desirable outcome for many many cases of engineering design (e.g., the rate at which a door opens or closes)

- Two real poles at $-\sigma$.
- Response: the sum of two scaled exponentials of the same time constant, one scaled to time.
- Solution: $f(t) = k_1 e^{-\sigma t} + k_2 t e^{-\sigma t}$

10.3.4 Overdamped systems

When $\zeta > 1$, a system in does not oscillate and decays at a slower rate than the critical case.

- Two real poles at $-\sigma_1$ and $-\sigma_2$.
- Response: sum of two exponentials with different time constant
- Solution: $f(t) = k_1 e^{-\sigma_1 t} + k_2 e^{-\sigma_2 t}$

10.4 “Inverting” the Laplace transform

$$\mathcal{L}\{f\}(s) = \mathcal{L}\{f(t)\}(s) = \tilde{F}(s) \quad (10.12)$$

Mellin’s inverse formula An integral formula for the inverse Laplace transform, called the Mellin’s inverse formula, the Bromwich integral, or the FourierMellin integral, is given by the line integral:

$$f(t) = \mathcal{L}^{-1}\{\tilde{F}(s)\} = \frac{1}{2\pi i} \lim_{T \rightarrow \infty} \int_{\gamma - iT}^{\gamma + iT} e^{st} \tilde{F}(s) ds, \quad (10.13)$$

where the integration is done along the vertical line $\text{Re}(s) = \gamma$ in the complex plane such that γ is greater than the real part of all singularities of $F(s)$ and $F(s)$ is bounded on the line, for example if contour path is in the region of convergence. If all singularities are in the left half-plane, or $F(s)$ is an entire function, then γ can be set to zero and the above inverse integral formula becomes identical to the inverse Fourier transform.

In practice, computing the complex integral can be done by using the Cauchy residue theorem. Or simply by recognizing common forms.

10.4.1 A convenient way of doing it

To find solutions to the equations left behind after we have transformed them via Laplace, I personally prefer to use the “cover-up method”.

Returning to our function describing current throughout the circuit

$$\tilde{I} = \frac{s - 10}{(s + 2)(s + 5)} \quad (10.14)$$

10.5 Worksheet

10.5.1 Problem 1

Find the Laplace transform of the following:

- $f(t) = 9$
- $f(t) = \delta(t)$ the Dirac-delta function
- $f(t) = e^{-3t/2}$
- $f(t) = \sin \omega t$

Solution

10.5.2 Problem 2

What is the differential equation describing an inductor, a resistor, and a capacitor in series?

Solution

10.5.3 Problem 3

What is the differential equation describing an inductor, a resistor, and a capacitor in series? What is a solution to that differential equation if $L = 1$ H, $R = 1 \Omega$, and $C = 100$ mF? Take the Laplace transform of the differential equation. What are its poles and zeros?

Solution

10.5.4 Problem 4

Draw an s-plane. Label the axes. Plot the poles and zeros you found. What can you say of the behavior of the system? If the poles had an imaginary component to them (that is, if they were pushed along the vertical axis), how would that affect our system?

10.5.5 Problem 5

Draw an s-plane. Label the axes. Plot these poles – $(-2,0)$ and $(-5,0)$ – and this zero – $(0,0)$. Plot what the signal would look over time at each of these poles and zeros.

Chapter 11

Circuits as ODEs: I. First-order

02/21/2019 Lecture 12.

11.1 Source-free RC circuits

11.1.1 One resistor, one capacitor

11.1.2 Two or more resistors and/or capacitors

11.2 Source-free “active” circuits

11.3 First-order systems with sources

11.4 Several singular functions

11.4.1 Unit step function, $u(t - t_0) = 1, t > t_0$

The Laplace transform of the unit step function

11.4.2 Unit impulse function, $\delta(t) = du(t)/dt$

Its “sifting” abilities

The Laplace transform of the unit impulse function

11.4.3 Unit ramp function, $r(t) = \int u(t)dt$

The Laplace transform of the unit impulse function

Chapter 12

Circuits as ODEs: II. Second-order

02/26/2019 Lecture 13.

12.1 A series RLC circuit

Chapter 13

System response: I. Convolution

02/28/2019

Contents

13.1 An introduction to thinking in systems	114
13.2 Pulse and impulse	114
13.3 Convolution	115
13.3.1 Convolution as a series of weighted sums	118
13.3.2 A few properties of convolution	118
13.3.3 The Laplace transform of a convolution	118
13.4 A few examples	119
13.4.1 Convolution of an exponential and a sin function .	119

13.1 An introduction to thinking in systems

Completely characterizing the input v. output properties of a system by exhaustive measurement of all parameters involved is usually not possible. As

13.2 Pulse and impulse

We have previously noted that the unit impulse function

$$\delta(t) = \begin{cases} \infty, & t = 0 \\ 0, & t \neq 0 \end{cases} \quad (13.1)$$

But another useful way of conceiving of the impulse signal is as a limiting case of the “pulse signal”, $\delta_\Delta(t)$:

$$\delta_\Delta(t) = \begin{cases} \frac{1}{\Delta}, & \text{if } 0 < t < \Delta \\ 0, & \text{otherwise} \end{cases} \quad (13.2)$$

It can be seen without much effort that the impulse signal is equal to the pulse signal when the pulse gets infinitely short.

It may also be helpful to consider integration at this point as a limiting case of summation:


$$\int_{t=-\infty}^{\infty} x(t)dt = \lim_{\Delta \rightarrow 0} \sum_{k=-\infty}^{\infty} x(k\Delta)\Delta \quad (13.3)$$

This even allows us to perhaps more easily reckon that the unit step signal can be obtained by integrating the unit impulse

$$u(t) = \int_{-\infty}^t \delta(\tau)d\tau \quad (13.4)$$

Well, as it turns out, any signal can be expressed as a sum of scaled and shift unit impulses. Indeed, thanks to our digital world, this is indeed how it mostly works out there in the real world, wherein discrete samples from an original signal may be approximated more or less exactly as pulse signals scaled to the amplitude of the sample. Mathematically,
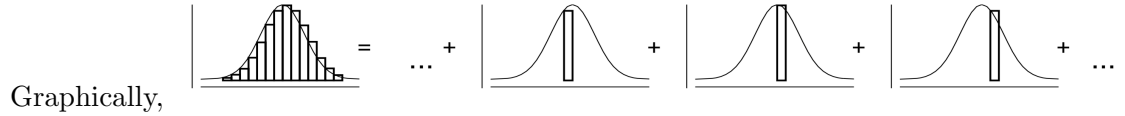
$$x(t) \approx \sum_{k=-\infty}^{\infty} x(k\Delta)\delta_\Delta(t - k\Delta)\Delta \quad (13.5)$$



As we let $\Delta \rightarrow 0$, our approximation of $x(t)$ hones in on reality with the summation approaching an integral and the pulse approach the unit impulse:

$$x(t) = \int_{-\infty}^{\infty} x(\tau)\delta(t - \tau)d\tau \quad (13.6)$$

Thus, we can represent any signal as an infinite sum of shifted and scaled unit impulse. This is indeed that best way we human beings have thus far figured out how to store information. A train of 1s and 0s.

13.3 Convolution

Recall, the two principles of linearity inherent in our studies here: **homogeneity** which enables the scaling of linear systems and **additivity** which allows us to sum up two or more linear systems. From these we arrive at the emergent phenomenon of **superposition** which states that $T(ax_1 + bx_2) = aT(x_1) + bT(x_2)$.


There is also a facet of these systems known as **shift-invariance** in which we say that so long as we don't (cause long-term) damage (to) a system by inputting some signal, then whether we input that signal at a time t or a time $t + \tau$ some while later will not significantly alter the response of the system. Such systems are said to be shift-invariant, and we will consider their behaviors here.¹

To characterize a linear, shift-invariant, one need only measure how a system responds to a unit impulse. This response is known as the **impulse response function** and in principle it allows us to predict how a system will respond to any other possible stimulus.


Graphically, this may be easy to understand. We can imagine that an impulse given to some system cause it to rapidly rise, then decay (exponentially) away. If we do this for ever point in time for a system of interest, we could fully characterize the total response of the system.

¹A shift-invariant system is the discrete equivalent of the time-invariant systems we have heretofore concerned ourselves with.


Impulses

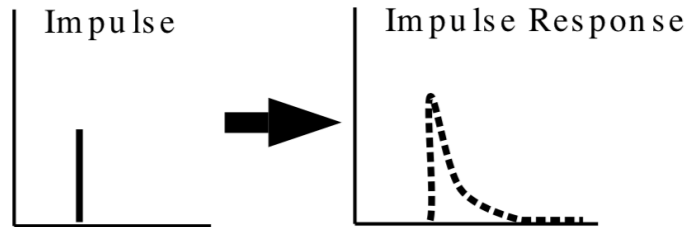

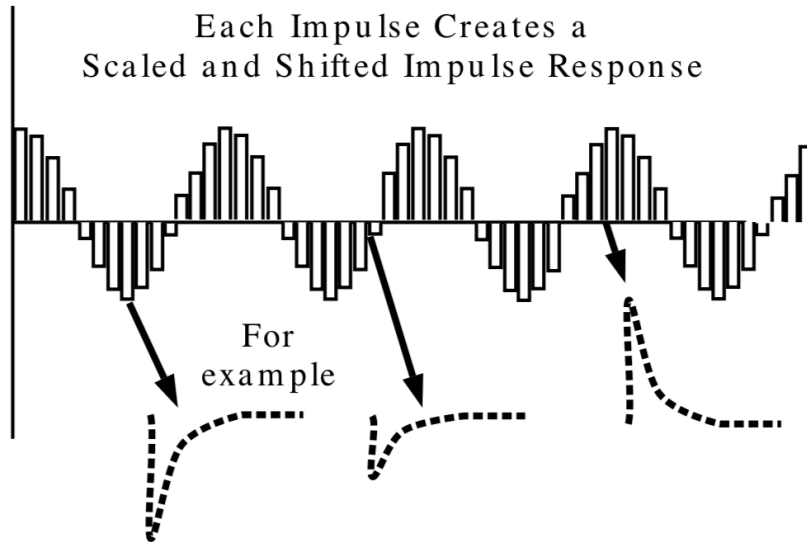Each Impulse Creates a
Scaled and Shifted Impulse Response



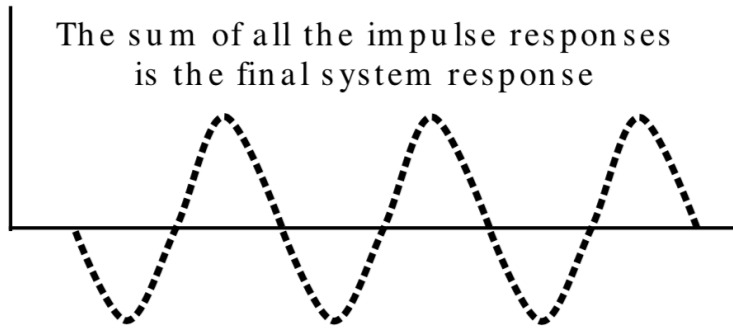The sum of all the impulse responses
is the final system response



Mathematically, we can call upon our two principles of linearity to guide our way. Let us define some output, $y(t)$, of a system, characterized by

transfer function², T , and an input signal, $x(t)$

$$y(t) = T[x(t)] = T\left(\int_{-\infty}^{\infty} x(\tau)\delta(t-\tau)d\tau\right) \quad (13.7)$$

$$= T\left(\lim_{\Delta \rightarrow 0} \sum_{k=-\infty}^{\infty} x(k\Delta)\delta_{\Delta}(t-k\Delta)\Delta\right) \quad (13.8)$$

From additivity,

$$y(t) = \lim_{\Delta \rightarrow 0} \sum_{k=-\infty}^{\infty} T(x(k\Delta)\delta_{\Delta}(t-k\Delta)\Delta) \quad (13.9)$$

Taking the limit,

$$y(t) = \int_{-\infty}^{\infty} T(x(\tau)\delta(t-\tau))d\tau \quad (13.10)$$

Homogeneity suggests:

$$y(t) = \int_{-\infty}^{\infty} x(\tau)T(\delta(t-\tau))d\tau \quad (13.11)$$

If we then define for ourselves the response of T to the unshifted unit response $h(t) = T[\delta(t)]$, then via shift-invariance we are left with

$$y(t) = \int_{-\infty}^{\infty} x(\tau)h(t-\tau)d\tau \quad (13.12)$$

This last result is worth sitting down and thinking about. Its consequence is that for any shift-invariant system, T , once we know its impulse response, we know how it will respond to every other system, since every other signal is merely a combination of scaled and shifted impulses.



This way of combining signals is so widespread and useful that it has its own mathematical shorthand, “*”, known as convolution. For any two signals, x and y , an output, $z(t)$, may be found by convolving x with y

$$z(t) = x * y = \int_{-\infty}^{\infty} x(\tau)y(t-\tau)d\tau \quad (13.13)$$

One way of thinking about this operation is it is as if you took two signals, left one where it was, put there at one side of eternity and found the piecewise multiplication and sum of two signals as you moved the other signal to the other side of eternity.

²It has helped some students to think of a “transfer” function merely as a “transform” function such that given an input, $x(t)$, there exists an output, $y(t)$, which is mapped from $x(t)$ via the transform, T .

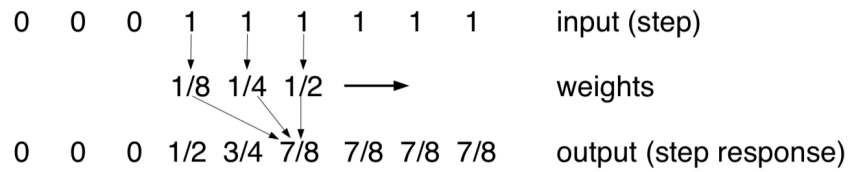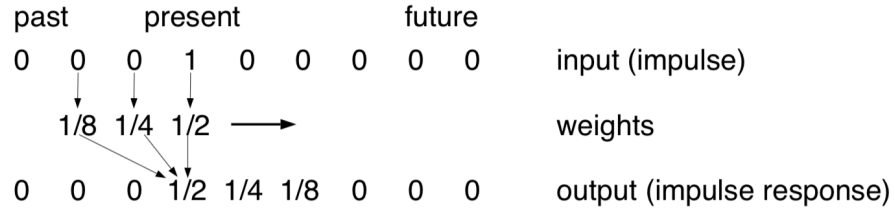13.3.1 Convolution as a series of weighted sums



The output of convolution may be thought of as a series of weight sums. More specifically, a linear, shift-invariant system will output a response that is a weighted sum of the inputs. That *weighting function* which helps maps the inputs to the output is very closely related to the impulse response of the system. Indeed, the impulse response and weighting function are time-reversed copies of each other (as shown in the top part of the graph).

13.3.2 A few properties of convolution

- Commutative: $x * y = y * x$
- Associative: $(x * y) * z = x * (y * z)$
- Distributive: $(x * z) + (y * z) = (x + y) * z$

13.3.3 The Laplace transform of a convolution

To editorialize a bit, perhaps the single most important thing to get out of this chapter is that convolution in the time-domain is the same as multiplication in the s -domain. That is

$$\mathcal{L}(f * g) = \tilde{F}(s) \cdot \tilde{G}(s) = \tilde{G}(s) \cdot \tilde{F}(s) = \mathcal{L}(g * f) \quad (13.14)$$

13.4 A few examples

Convolution of two functions.

Find the convolution of $f(t) = e^{-t}$ and $g(t) = \sin(t)$.

Integrate by parts twice: $\int_0^t e^{-\tau} \sin(t-\tau) d\tau =$

$$2 \int_0^t e^{-\tau} \sin(t-\tau) d\tau = \left[e^{-\tau} \cos(t-\tau) \right]_0^t - \left[e^{-\tau} \sin(t-\tau) \right]_0^t$$

We conclude: $(f * g)(t) = \frac{1}{2}[e^{-t} + \sin(t) - \cos(t)]$. ◀



${}^3\text{0}^-$ and t^+ will be avoided in this derivation for convenience, but the interested reader is encouraged to redo this proof with their inclusion. It should come out the same

Chapter 14

System response: II. Stability

03/12/2019 Lecture 15.

14.1 An introduction

14.1.1 What do we mean by stability?

14.2 Undamped, $\zeta = 0$

14.3 Underdamped, $0 < \zeta < 1$

14.4 Overdamped, $\zeta > 1$

Part III

& Signals

Chapter 15

System response: III. The frequency domain

03/14/2019 Lecture 16.

Chapter 16

System response: IV. Filters

03/19/2019 Lecture 17.

Chapter 17

System response: V. Feedback; Homework IV

03/21/2019 Lecture 18.

Exam II

03/26/2019

Part IV

in Biomedical Engineering

Chapter 18

Bioelectricity: I. Passive properties

03/28/2019 Lecture 19.

18.1 Modeling biological material with a simple circuit, $R_1 + (R_2 || C)$

18.2 Resistance-Reactance Plane

18.3 What can we do with this information?

Chapter 19

Bioelectricity: II. Active properties

04/02/2019 Lecture 20.

Chapter 20

Bioelectricity: III. Measurement

04/04/2019 Lecture 21.

Chapter 21

Digital circuits: I. Discretization

04/09/2019 Lecture 22.

Chapter 22

Digital circuits: II. Logic; Homework V

04/11/2019 Lecture 23.

Chapter 23

Happenstance: A few BME specific situations

04/16/2019 Lecture 24.

Chapter 24

Circumstance: A few BME specific standards

04/18/2019 Lecture 25.

Chapter 25

A philosophy of circuits, systems, and signals; Homework VI

04/23/2019 Lecture 26.

Exam III

04/26/2019, 4:00-6:00pm

Part V

Assignments

Homework I

Assigned January 22, 2019. Due January 31, 2019 as *both* a hard copy in class and a pdf on Canvas. Each problem worth 10 points.

1.1 Problem 1

(15 points) A typical automated external defibrillator (AED) delivers 200-1000 V in less than 10 ms.

1. If the AED in front us delivers a pulse of 600 V, how much current is needed to deliver 120, 240, and 360 Joules?
2. Assuming two human hands have a mass of approximately 1 kg, how many chest compressions would be needed to deliver an equivalent amount of energy if each compression had a depth of 5 cm and was delivered at a constant speed of 0.5 m/s every 2 seconds?
3. If you had the option of having your heart jump-started would you choose an AED or the bare hands of a stranger? Justify your answer.

1.2 Problem 2

(5 points) A 3.3 V battery you are considering for a wearable you are designing has a total charge of 300 mAh. How many joules is this battery capable of delivering?

1.3 Problem 3

(5 points) A fellow engineer bought a 12 V battery rated for 60 Ah. The experiment you both have in mind will draw 2 A over a 1 k Ω load. How long can your experiment last?

1.4 Problem 4

(5 points) A piece of medical equipment supplies 135 W at 220 V. How much electrical charge flows through the device in the 10 hours a nurse is on-call using it? And how many electrons does this charge correspond to?

1.5 Problem 5

(10 points) During an in vitro (petri dish) experiment, the peak electric power that a group of stem cells can tolerate without some serious functional consequence is known to have a threshold of about 1 mW. If the power delivered to this group of cells is defined as $p(t) = 2e^{-t} \sin 5t$ [mW], will the cell be harmed and if so how long can power be delivered before the cells are harmed?

1.6 Problem 6

(10 points) Find the equivalent resistances. (Show your work.)

- 1 square of resistors ($R = 10 \text{ k}\Omega$) measured across corners.
- 2 resistors ($R_1 = 10 \text{ k}\Omega$, $R_2 = 4 \text{ k}\Omega$) in series.
- 3 resistors ($R_1 = R_2 = R_3 = 10 \text{ k}\Omega$) in parallel.
- 4 resistors ($R_1 = 1 \text{ k}\Omega$, $R_1 = 2 \text{ k}\Omega$, $R_1 = 3 \text{ k}\Omega$, $R_1 = 4 \text{ k}\Omega$) in parallel.
- 5 resistors ($R = 10 \text{ k}\Omega$) in a pentagon, measured across each resistor.

1.7 Problem 7

(10 points) Hospitals often employ what is known as a dynamic uninterruptible power system (D-UPS) comprising a diesel generator, a synchronous machine, and a kinetic energy unit. By way of example, if the energy to a particular hospital fails, the kinetic energy unit continues to feed 600 kW to the hospital for 20 seconds, allowing the generator and synchronous machine to take over and feed the load.

1. What is the total energy capacity of this kinetic energy unit?
2. If the hospital were operating at 240 kW (instead of the aforementioned 600 kW), how much longer can the unit feed the load?

1.8 Problem 8

(10 points) Current passing through an electrical element in an AC situation can generally be defined as $i(t) = A \sin \omega t$.

1. Determine the energy on this element if the voltage across it is $v(t) = B \cos \omega t$.
2. Plot current, voltage, and energy as functions of time using MATLAB (or an equivalent software package). You may use any values of A , B , and ω that you'd like, but unit values ($=1$) might make your life/work easier. (Present the code you used to arrive at your plot.)


1.9 Problem 9

(10 points) The materiality of the human body ensures that it puts up some resistance to the flow of current. Find some values of impedance for the following human body parts. Be sure to cite your source(s) and explain why you trust it. (Given that there is a frequency dependence to these values, you may present any value of impedance found between 1 — 100 kHz.)

1. The whole body, from head to toe.
2. A single limb (such as an arm or a leg).
3. Blood.
4. Muscle.
5. Fat.

1.10 Problem 10

(20 points) For the circuit shown below.

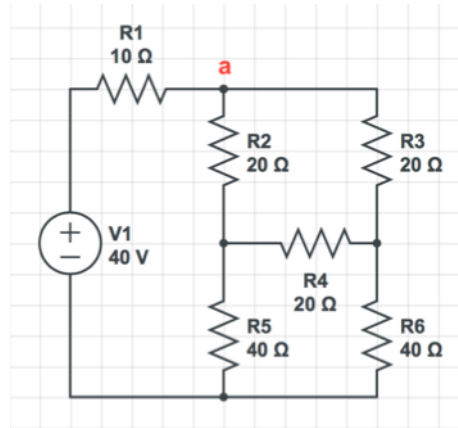


1. Use the delta-wye transformation rule to determine the power dissipated by R_1 .
2. Find the voltage at node a (just after R_1).
3. If R_4 were changed to $100\ \Omega$, would the results to (10.1) and/or (10.2) change? How do you know?
4. How many nodes, branches, and loops are there?
5. What is the voltage at each node, the current through each branch?

Homework II

Assigned February 8, 2019. Due February 14, 2019 as *both* a hard copy in class and a pdf on Canvas. Each problem worth 10 points.

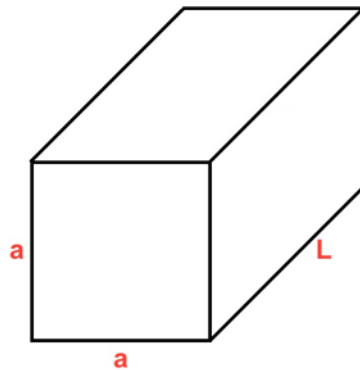2.1 Problem 1


Though we rarely think about it, resistors have a directionality to them. To prove this to ourselves, let us consider a rectangular prism with a square cross-sectional area with a width of a on its square face, a length of L , and a resistivity of ρ . An example of such a conductor may be seen in the figure below.



1. Determine the resistance between two parallel square faces, two parallel rectangular faces, and determine the ratio of these two resistances.
2. How would you go about performing a similar analysis for a resistor with a circular cross-sectional area?

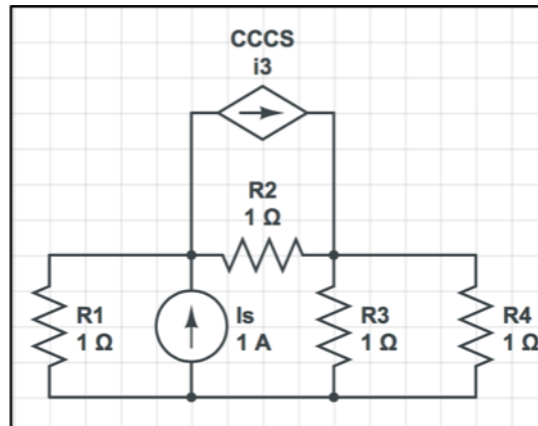
2.2 Problem 2

For the circuit shown below, find the current flowing through R_3 (i_3) and the current flowing through R_4 (i_4).



2.3 Problem 3


For the circuit shown below.

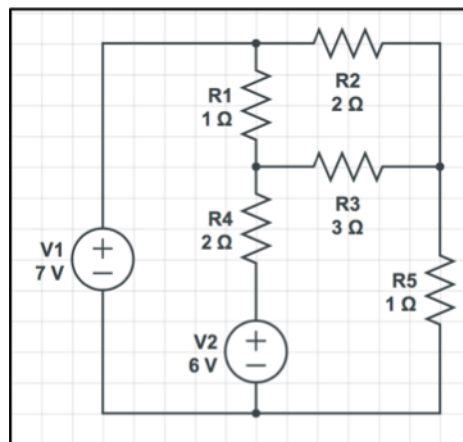

1. Perform a mesh analysis and determine the mesh currents in each loop. (You may solve it any way you'd like, just walk me through how you solve it.)
2. Determine the current through R_3 . How would you actually measure the actual current through R_3 in an actual circuit?

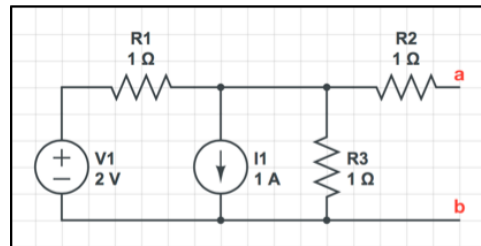
2.4 Problem 4

For the circuit shown below, determine the Thvenin and Norton equivalent circuits between terminals a and b.



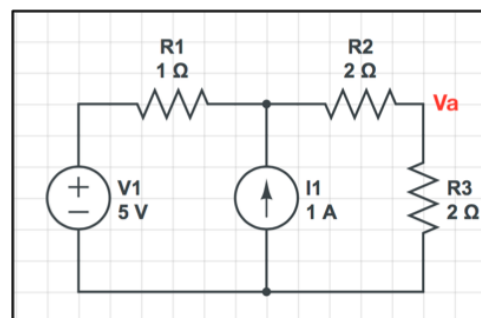
2.5 Problem 5

Using the superposition theorem, find the voltage V_a in the circuit shown below. Be sure to show all your steps.



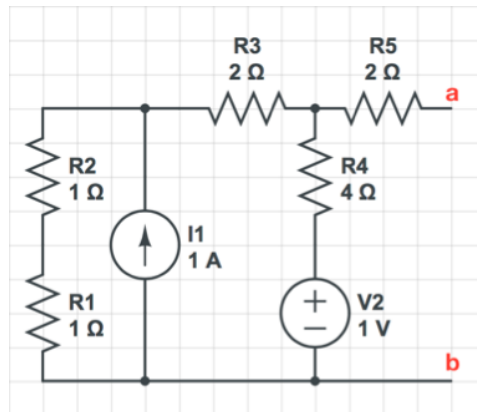2.6 Problem 6

For the circuit shown below, determine the Thvenin equivalent circuit that would be found between the **a** and **b** terminals.




2.7 Problem 7

Electrocardiographic (ECG) signals tend to be about 1 mV before being measured by a monitoring system (that is, it is about 1 mV just before it gets to our skin). If skin resistance is about $100\text{ k}\Omega$, what is the voltage as measured by our system if our system has an input impedance of $500\text{ k}\Omega$, $1\text{ M}\Omega$, and $2\text{ M}\Omega$. You may model the entire situation as a series combination of elements. What effect do you think sweating at the area of measurement will have on the voltages you just calculated?

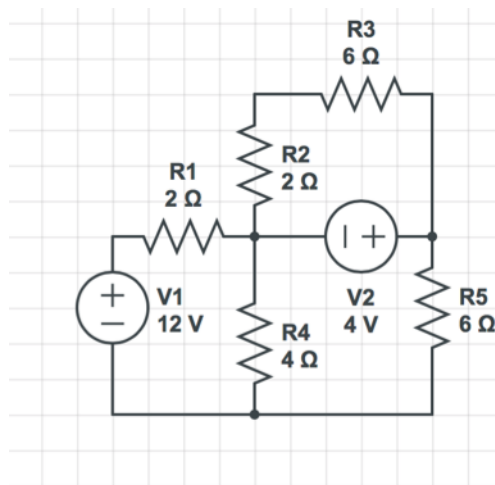2.8 Problem 8

For the circuit below, find the current passing through each element.



2.9 Problem 9

Our blood vessels are something of glorified hollow conductive cylinders. Let us assume that the resistivity of the vessel, ρ , is constant throughout our length of interest, L . If we were to apply a potential difference, V , between the inner surface of the blood vessel (with radius a) and the outer surface of the blood vessel (with radius b), what would be the resistance we measure? (Hint: the differential resistance in this case is equal to $dR = \rho(dL/A)$.)

2.10 Problem 10

To the extent you feel comfortable sharing this information, have you ever had to interact with a piece of biomedical equipment that utilized electronic circuitry? (This may include anything from a Fitbit to an ECG and beyond.) If so, what aspects of that experience relating to the equipment did you find fascinating, and which aspects of it would you personally liked to have seen improved? [If you do not wish to share a personal experience or perhaps do not have one to share, consider the question in the abstract: *knowing what you know, what might you wish to see improved regarding current medical instruments?*]

Homework III

Assigned February 22, 2019. Due February 28, 2019 as *both* a hard copy in class (at the beginning thereof) and a pdf on Canvas (by 11:59pm). Each problem worth 20 points.

3.1 Problem 1 on mathematical proficiency

Please find the Laplace transforms for the following functions. Be sure to show as much of your work as you can. And please also resist the urge to use computational means of finding these answers. Try it yourself! It's good exercise.

1. $a(t) = \sin(\omega t)$
2. $b(t) = \cos(\omega t)$
3. $c(t) = 1 - \cos(\omega t)$
4. $d(t) = t$
5. $f(t) = t^n$

3.2 Problem 2 on poles and zeros, exponentially

Find the poles and zeroes of the following functions. Again, show as much of your work as you can and resist those computational urges.

1. $f(t) = e^{-3t}$
2. $f(t) = e^{-3t-2t+1t} \cdot e^{-t}$
3. $f(t) = e^{-3t} \cdot \sin(3t)$
4. $f(t) = e^{-3t} \cdot \cos(4t - 3t)$
5. $f(t) = e^{3t} \cdot e^{-2t} \cdot \sin(t) \cdot \cos(-t)$

3.3 Problem 3 on the stability of geopolitical systems

“Stability” is a property we seek in many systems. Representing something of a “back of the envelope” approximation of the time course of geopolitical entities, a model was first proposed by a fellow by the name of Lewis Fry Richardson to track the development of weapons used/accrued by the nations of the earth. Richardson’s Arms race, expressed as the coupled differential equation below, relates the rate at which one country (Country 1) develops its arms, dx/dt to the rate at which another country (Country 2) develops its arms dy/dt :

$$\frac{dx}{dt} = Ay - mx \tag{3.1}$$


$$\frac{dy}{dt} = Bx - ny \tag{3.2}$$

One can see that these rates are proportional to the the amount of arms the other country has minus the amount of arms the country has. If we know that $s < 0$ for a system to be stable, determine the conditions of stability in this system. (Assume the world starts peacefully with no weapons in either country.) Comment on the results.

3.4 Problem 4 on a circuit as a differential equation


For circuit below

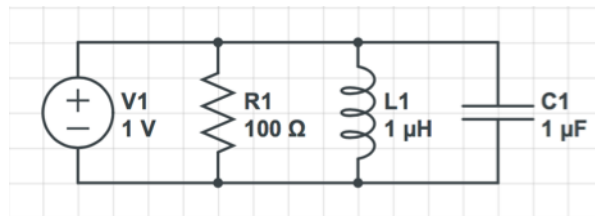1. Write its differential equation and take its Laplace transform (assume all initial conditions are equal to zero).
2. Find its transfer function (the ratio of voltage to current).
3. Choose **five** triplets of values (different from those printed on the figure). Plot the output of each transfer function as *either* a function of time (t) or frequency ($s = j\omega$).



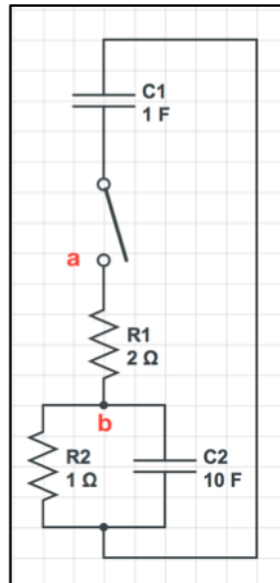3.5 Problem 5 on poles and zeros, applicably

Believe it or not, this Laplace and circuitry stuff can actually be useful to those more biologically inclined among us. Indeed, it can be used to describe how drugs perfuse into our bodies. Let us consider taking some drugs.¹ We may model the drug as a charged capacitor, $C1$, with a potential of 100 V across it and a value of 1 F. Recalling that the tissues within our bodies may be modeled as the combination of a resistor, $R1$, in series with the parallel combination of a resistor, $R2$, and a capacitor, $C2$, we may model the perfusion of the drug within the body as the time rate of change of potential within the circuit shown at right. Once weve taken the drug ($t = 0$), the switch is closed. Using nodal analysis, determine the potential at point b in the s-domain. What are the poles of this model?



¹Don't do drugs, kids.